

ASSIGNMENT 4

Name: Ishan thakkar

ID NO.: - 21EL032

Division: - 04

Year: - 2023-24

Subject: - Digital System Design (3EL42)

Branch: - Electronics (EL)

1 BCD TIMECOUNT

Verilog code:-

```
module BCD_TimeCounter(  
    input wire clk,    // Clock input  
    input wire rst,    // Reset input  
    output reg [3:0] bcd_seconds, // BCD representation of seconds  
    output reg [3:0] bcd_minutes, // BCD representation of minutes  
    output reg [3:0] bcd_hours   // BCD representation of hours  
);  
  
reg [3:0] seconds;  
reg [3:0] minutes;  
reg [3:0] hours;
```

```

always @(posedge clk or posedge rst) begin
    if (rst) begin
        seconds <= 4'b0000;
        minutes <= 4'b0000;
        hours <= 4'b0000;
    end else begin
        seconds <= (seconds == 4'b1001) ? 4'b0000 : seconds + 4'b0001;
        if (seconds == 4'b0000) begin
            minutes <= (minutes == 4'b1001) ? 4'b0000 : minutes + 4'b0001;
            if (minutes == 4'b0000) begin
                hours <= (hours == 4'b1001) ? 4'b0000 : hours + 4'b0001;
            end
        end
    end
end
end

```

```

always @(*) begin
    bcd_seconds = seconds;
    bcd_minutes = minutes;
    bcd_hours = hours;
end

```

endmodule

Testbench:-

```

module BCD_TimeCounter_Testbench;
    reg clk;
    reg rst;
    wire [3:0] bcd_seconds;

```

```
wire [3:0] bcd_minutes;
```

```
wire [3:0] bcd_hours;
```

```
BCD_TimeCounter uut (  
    .clk(clk),  
    .rst(rst),  
    .bcd_seconds(bcd_seconds),  
    .bcd_minutes(bcd_minutes),  
    .bcd_hours(bcd_hours)  
);
```

```
initial begin
```

```
    clk = 0;
```

```
    rst = 0;
```

```
    rst = 1;
```

```
    #10 rst = 0;
```

```
    repeat (100) begin
```

```
        #5 clk = ~clk;
```

```
    end
```


```
    $display("Time: %d%d:%d%d:%d%d", bcd_hours, bcd_hours, bcd_minutes, bcd_minutes,  
bcd_seconds, bcd_seconds);
```

```
    $finish;
```

```
end
```

```
endmodule
```

RTLsymatic:-

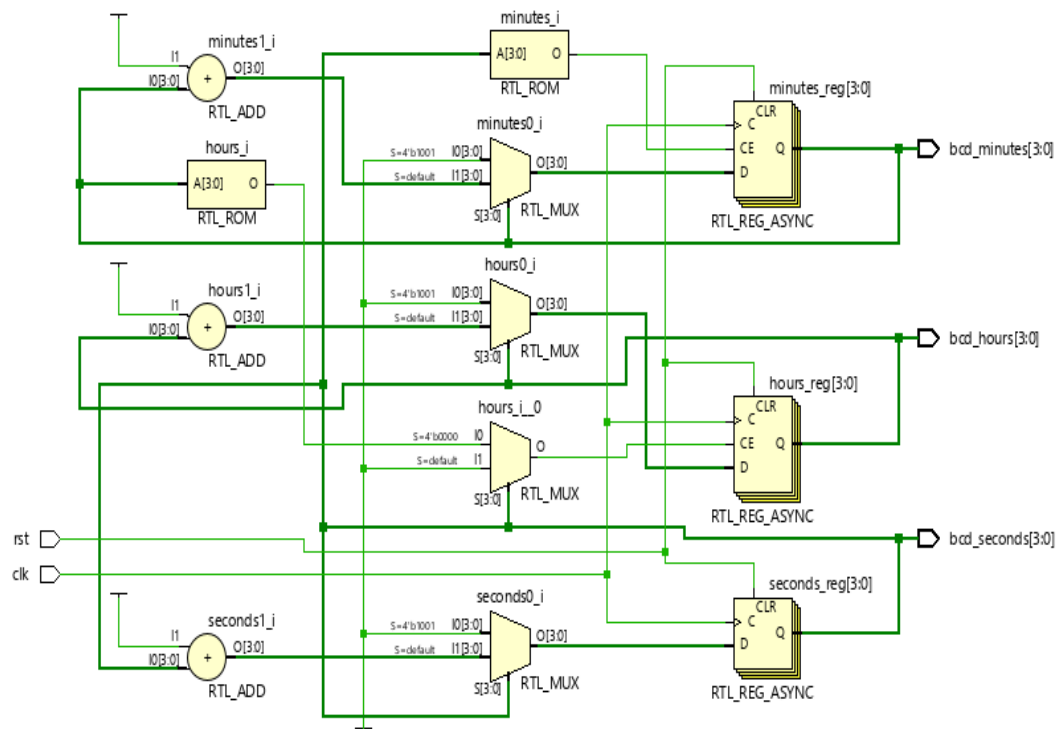

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
| BlackBox name |Instances |
+-----+
+-----+

```

Report Cell Usage:

```

+-----+
| Cell |Count |
+-----+
+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:31 ; elapsed = 00:00:35 . Memory (MB): peak = 1020.398 ; gain = 0.078


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.945 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 49.4°C
Thermal Margin: 75.6°C (12.1 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

2 3-1 MUX

Verilog code:-

```
module mux3to1(  
    input wire a,  
    input wire b,  
    input wire c,  
    input wire sel,  
    output wire y  
);
```

```
    assign y = (sel == 2'b00) ? a :  
               (sel == 2'b01) ? b :  
               (sel == 2'b10) ? c :  
               (sel == 2'b11) ? 1'b0 : 1'bx;
```

Endmodule

Testbench:-

```
module testbench_mux3to1;
```

```
reg a, b, c, sel;
```

```
// Output
```

```
wire y;
```

```
mux3to1 uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .c(c),
```

```
    .sel(sel),
```

```
    .y(y)
```

```
);
```

```
initial begin
```

```
    a = 1'b0;
```

```
    b = 1'b1;
```

```
    c = 1'b1;
```

```
    sel = 2'b00;
```

```
#10 sel = 2'b01;
```

```
#10 sel = 2'b10;
```

```
#10 sel = 2'b11;
```

```
$finish;
```

```
end
```


```
always @(y) begin
```

```
    $display("y = %b", y);
```

```
end
```

```
endmodule
```

Rtl symatic:-

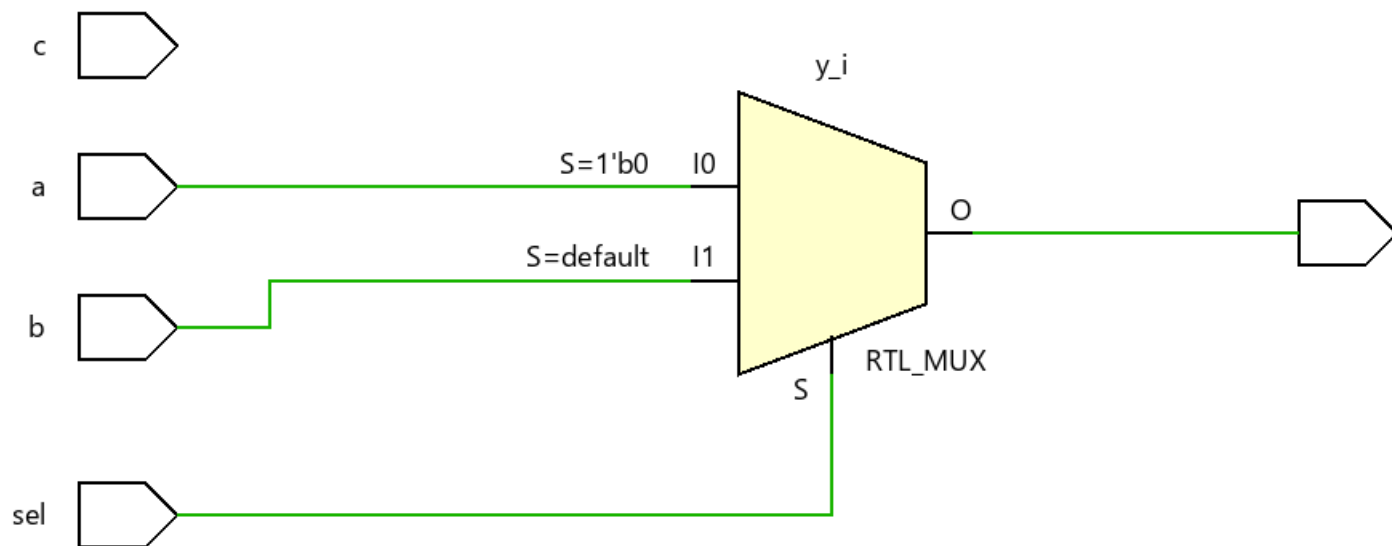

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
LUT3	1
IBUF	3
OBUF	1

Finished Writing Synthesis Report : Time (s): cpu = 00:00:21 ; elapsed = 00:00:24 . Memory (MB):


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.413 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	27.6°C
Thermal Margin:	97.4°C (15.6 W)
Effective θ_{JA} :	6.2°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

3 BCD TO SEVEN SEGMENT DISPLAY

Verilog code:-

```
module bcd_to_7seg(  
    input wire [3:0] bcd_in,  
    output wire [6:0] seg_out  
);
```



```
assign seg_out[0] = ~((bcd_in == 4'b0000) | (bcd_in == 4'b1000));
assign seg_out[1] = ~((bcd_in == 4'b0001) | (bcd_in == 4'b1001));
assign seg_out[2] = ~((bcd_in == 4'b0010) | (bcd_in == 4'b1010));
assign seg_out[3] = ~((bcd_in == 4'b0011) | (bcd_in == 4'b1011));
assign seg_out[4] = ~((bcd_in == 4'b0100) | (bcd_in == 4'b1100));
assign seg_out[5] = ~((bcd_in == 4'b0101) | (bcd_in == 4'b1101));
assign seg_out[6] = ~((bcd_in == 4'b0110) | (bcd_in == 4'b1110));
```

```
endmodule
```

Testbench:-

```
module testbench_bcd_to_7seg;
```

```
    reg [3:0] bcd_in;
```

```
    wire [6:0] seg_out;
```

```
    bcd_to_7seg uut (
        .bcd_in(bcd_in),
        .seg_out(seg_out)
    );
```

```
    initial begin
```

```
        $monitor("bcd_in = %b, seg_out = %b", bcd_in, seg_out);
```

```
        bcd_in = 4'b0000;
```

```
        #10 bcd_in = 4'b0001;
```

```

#10 bcd_in = 4'b0010;
#10 bcd_in = 4'b0011;
#10 bcd_in = 4'b0100;
#10 bcd_in = 4'b0101;
#10 bcd_in = 4'b0110;
#10 bcd_in = 4'b0111;
#10 bcd_in = 4'b1000;
#10 bcd_in = 4'b1001;
#10 bcd_in = 4'b1010;
#10 bcd_in = 4'b1100;
#10 bcd_in = 4'b1111;


$finish;

end

```

endmodule

Rtl symatic:-

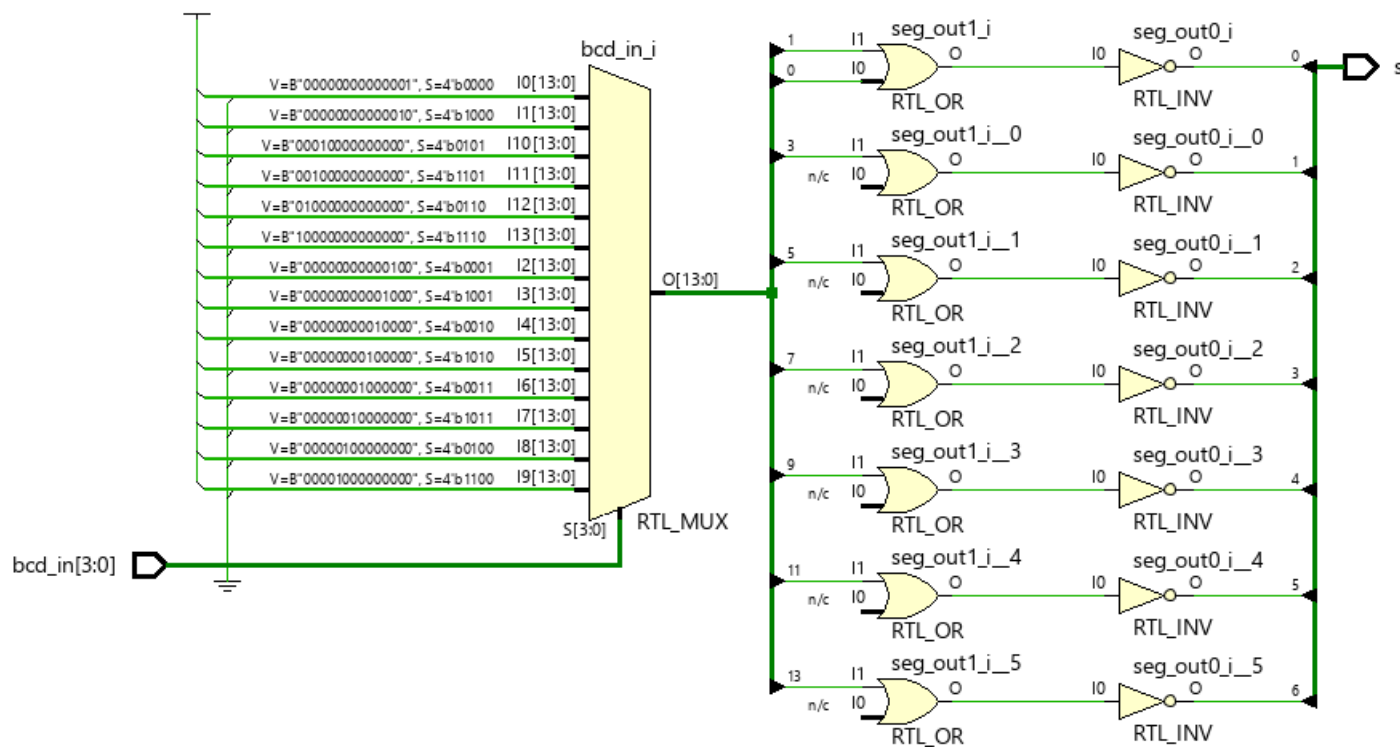

Synthesis report:-

```
-----  
Start Writing Synthesis Report  
-----
```

```
Report BlackBoxes:
```

```
+--+-----+-----+  
| |BlackBox name |Instances |  
+--+-----+-----+  
+--+-----+-----+
```

```
Report Cell Usage:
```

```
+-----+-----+-----+  
|      |Cell |Count |  
+-----+-----+-----+  
|1      |LUT3 |    7 |  
|2      |IBUF |    3 |  
|3      |OBUF |    7 |  
+-----+-----+-----+
```

```
-----  
Finished Writing Synthesis Report : Time (s): cpu = 00:00:19 ; elapsed = 00:00:25 . Memory (MB) :  
-----
```


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.212 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 32.5°C
Thermal Margin: 92.5°C (14.8 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

4 D LATCH USING 2:1 MUX

Verilog code:-

```
module d_latch_with_mux (  
    input wire D,
```

```
    input wire E,  
    output wire Q  
);
```

```
wire W;  
assign W = (E) ? D : Q;
```

```
assign Q = W;
```

```
endmodule
```

Testbench:-

```
module testbench_d_latch_with_mux;
```

```
    reg D, E;
```

```
    wire Q;
```

```
    d_latch_with_mux uut (  
        .D(D),  
        .E(E),  
        .Q(Q)  
    );
```

```
    initial begin
```

```
        $monitor("D = %b, E = %b, Q = %b", D, E, Q);
```

D = 1'b0;

E = 1'b0;

#10 E = 1'b1;

D = 1'b1;

#10 E = 1'b0;

D = 1'b0;

#10 E = 1'b1;

D = 1'b1;

#10 E = 1'b0;


D = 1'b0;

\$finish;

end

endmodule

RTIsymatic:-

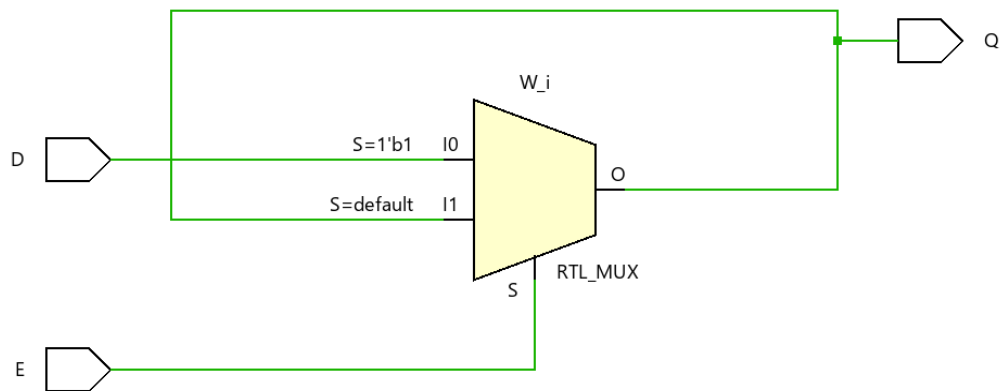

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+
| Cell |Count |
+-----+
|1| LUT3 | 1|
|2| IBUF | 2|
|3| OBUF | 1|
+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:21 ; elapsed = 00:00:23 . Memory (MB): peak = 1029.855 ; gain = 11.023

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.472 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 27.9°C
Thermal Margin: 97.1°C (15.5 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

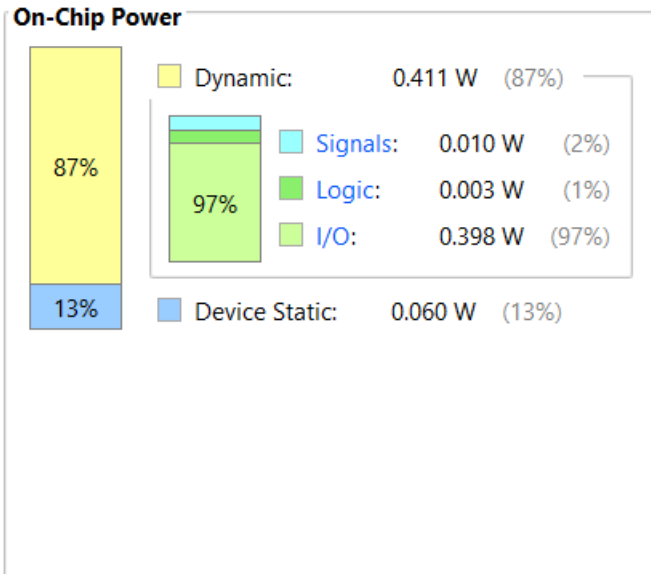[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



5 8-BIT BARREL SHIFTER

Verilog code:-

```
module barrel_shifter(  
    input wire [7:0] data_in, // Input data (8 bits)  
    input wire [2:0] shift_amount, // Shift amount (0 to 7)  
    input wire shift_left, // Shift direction (0: right, 1: left)  
    output wire [7:0] data_out // Output data (8 bits)  
);  
  
    assign data_out = (shift_left) ? (data_in << shift_amount) : (data_in >> shift_amount);  
  
endmodule
```

Testbench:-

```
module test_bench;  
    reg [7:0] data_in;  
    reg [2:0] shift_amount;  
    reg shift_left;  
    wire [7:0] data_out;
```

```
barrel_shifter uut (  
    .data_in(data_in),  
    .shift_amount(shift_amount),  
    .shift_left(shift_left),  
    .data_out(data_out)  
);
```

```
initial begin
```

```
    $display("Testing Barrel Shifter");
```

```
    data_in = 8'b11001100;
```

```
    shift_amount = 3'b001;
```

```
    shift_left = 1'b0;
```

```
    #10 $display("Data In: %b", data_in);
```

```
    $display("Shift Amount: %b", shift_amount);
```

```
    $display("Shift Direction: %b", shift_left);
```

```
    #10 $display("Data Out: %b", data_out);
```

```
    data_in = 8'b11001100;
```

```
    shift_amount = 3'b001;
```

```
    shift_left = 1'b1;
```

```
    #10 $display("Data In: %b", data_in);
```

```
    $display("Shift Amount: %b", shift_amount);
```

```
    $display("Shift Direction: %b", shift_left);
```

```
    #10 $display("Data Out: %b", data_out);
```



```


$finish;

end

endmodule

```

RTIsymatic:-

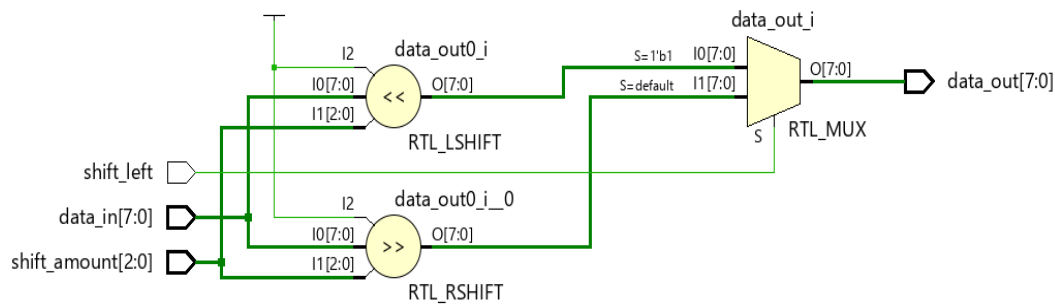

Synthesis report:-

```

Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | LUT3 | 4 |
| 2 | LUT4 | 4 |
| 3 | LUT5 | 6 |
| 4 | LUT6 | 10 |
| 5 | IBUF | 12 |
| 6 | OBUF | 8 |
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:25 . Memory (MB): peak = 1035.742 ; gain = 21.305

```

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.45 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 46.3°C

Thermal Margin: 78.7°C (12.6 W)


Effective θ_{JA} : 6.2°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

6 1-BIT COMPARATOR USING 4X1 MUX

Verilog code:-

```
module comparator_1bit(
    input wire a,
    input wire b,
    output wire equal
);
    wire a_inv;
    wire b_inv;
    wire ab_and;
    wire a_invb_and;

    assign a_inv = ~a;
    assign b_inv = ~b;

    assign ab_and = a & b;
    assign a_invb_and = a_inv & b;

    assign equal = (ab_and | a_invb_and);

endmodule
```

Testbench:-

```
module test_bench;
    reg a;
    reg b;
    wire equal;
    comparator_1bit uut (
        .a(a),
```

```

.b(b),
.equal(equal)
);

```

```

initial begin

```

```

    $display("Testing 1-Bit Comparator");

```

```

    a = 1'b0;

```

```

    b = 1'b0;

```

```

    #10 $display("a: %b, b: %b, Equal: %b", a, b, equal);

```

```

    a = 1'b0;

```

```

    b = 1'b1;

```

```

    #10 $display("a: %b, b: %b, Equal: %b", a, b, equal);

```

```

    a = 1'b1;

```

```

    b = 1'b0;

```

```

    #10 $display("a: %b, b: %b, Equal: %b", a, b, equal);

```

```

    a = 1'b1;

```

```

    b = 1'b1;

```

```

    #10 $display("a: %b, b: %b, Equal: %b", a, b, equal);

```

```

    $finish;

```

```

end


```

```

endmodule

```

RTLsymatic:-

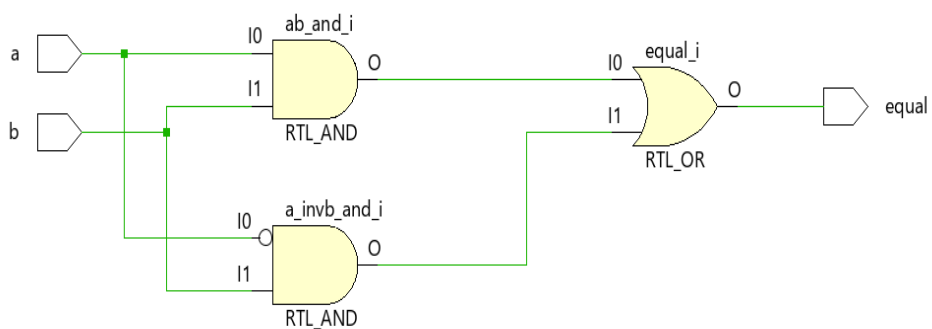

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
+-----+
```

Report Cell Usage:


```
+-----+
| Cell | Count |
+-----+
| 1 | IBUF | 1 |
| 2 | OBUF | 1 |
+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:24 . Memory (MB): peak = 1020.594 ; gain = 3.348

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

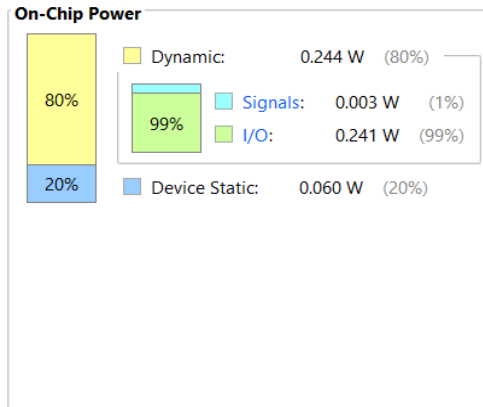Total On-Chip Power: 0.304 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.9°C
Thermal Margin: 98.1°C (15.7 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



7 LOGICAL, ALGEBRAIC, AND ROTATE SHIFT OPERATIONS


(1) Logical operation

Verilog code:-

```
module logical_shift(  
    input wire [7:0] data_in,  
    input wire [2:0] shift_amount,  
    input wire shift_left,  
    output wire [7:0] data_out  
);  
  
assign data_out = (shift_left) ? (data_in << shift_amount) : (data_in >> shift_amount);
```

endmodule

RtIsymatic:-

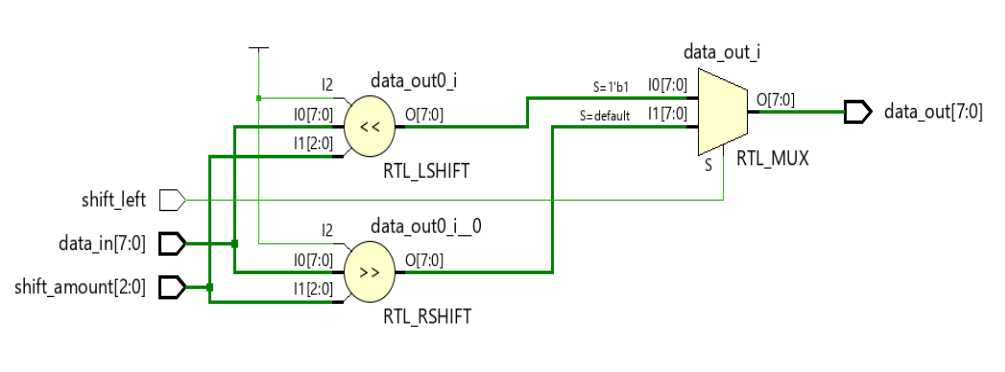

Synthesis report:-

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| LUT3 | 4|
|2| LUT4 | 4|
|3| LUT5 | 6|
|4| LUT6 | 10|
|5| IBUF | 12|
|6| OBUF | 8|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:21 ; elapsed = 00:00:24 . Memory (MB): peak = 1034.711 ; gain = 20.508
```

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.45 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 46.3°C


Thermal Margin: 78.7°C (12.6 W)

Effective θ_{JA} : 6.2°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

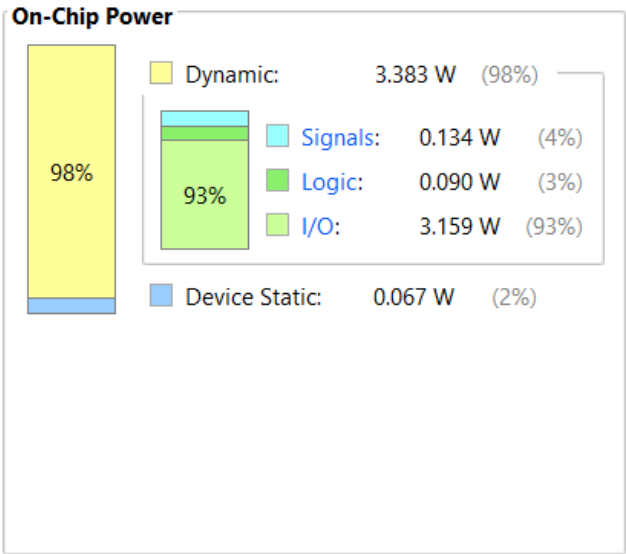[Launch Power Constraint Advisor](#) to find and fix invalid switching activity




(2)Algebraic shift

Verilog code:-

```
module algebraic_shift(  
    input wire [7:0] data_in,  
    input wire [2:0] shift_amount,  
    input wire shift_left,  
    output wire [7:0] data_out  
);  
  
    assign data_out = (shift_left) ? ((data_in << shift_amount) | ({8{data_in[7]}} <<  
shift_amount)) :  
        ((data_in >> shift_amount) | ({8{data_in[7]}} >>  
shift_amount));  
  
Endmodule
```

RTIsymatic:-

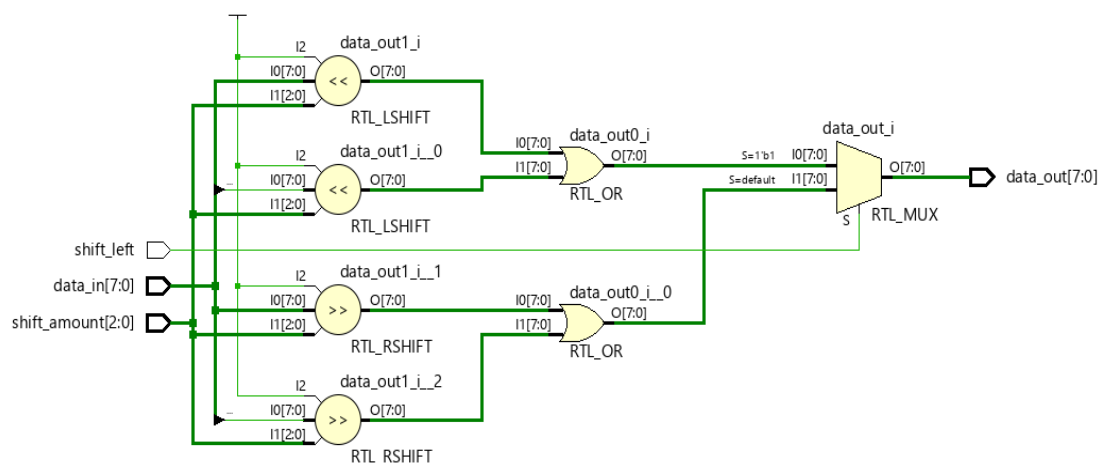

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+  
| BlackBox name | Instances |  
+-----+  
+-----+
```

Report Cell Usage:

```
+-----+  
| Cell | Count |  
+-----+  
|1| LUT4 | 7|  
|2| LUT5 | 11|  
|3| LUT6 | 10|  
|4| MUXE7 | 3|  
|5| IBUF | 12|  
|6| OBUF | 8|  
+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:19 ; elapsed = 00:00:25 . Memory (MB): peak = 1031.508 ; gain = 16.961

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.72 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 48.0°C
 Thermal Margin: 77.0°C (12.3 W)
 Effective θ_{JA} : 6.2°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

(3)Rotate shift:-


Verilog code:-

```
module rotate_shift(
    input wire [7:0] data_in,
    input wire [2:0] shift_amount,
    input wire shift_left,
    output wire [7:0] data_out
);

    assign data_out = (shift_left) ? (data_in << shift_amount) | (data_in >> (8 -
    shift_amount)) :
        (data_in >> shift_amount) | (data_in << (8 - shift_amount));

Endmodule
```

RTIsymatic:-

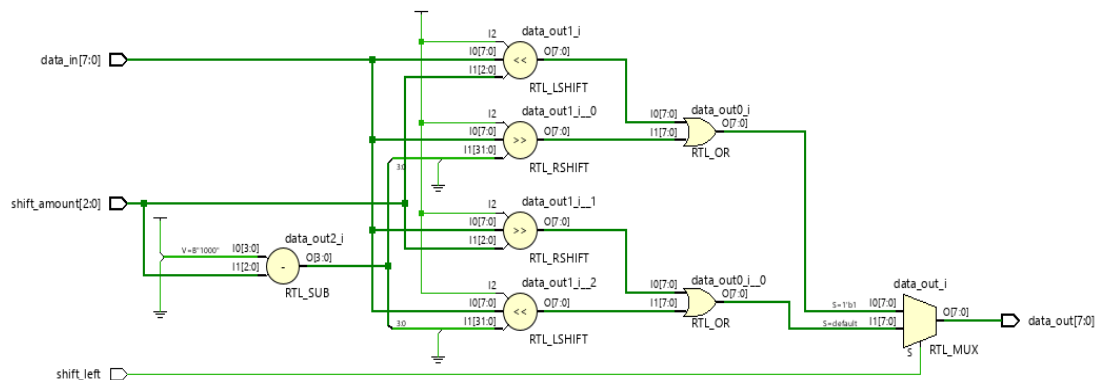

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
|BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:


```
+-----+
|Cell |Count |
+-----+
|1 |LUT6 | 24|
|2 |IBUF | 12|
|3 |OBUF | 8|
+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:25 . Memory (MB): peak = 1035.004 ; gain = 17.523

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

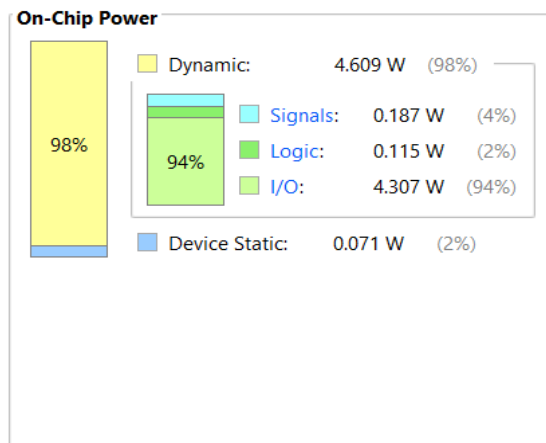Total On-Chip Power: **4.68 W**
Design Power Budget: **Not Specified**
Power Budget Margin: **N/A**
Junction Temperature: **53.9°C**
Thermal Margin: 46.1°C (7.4 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: **Low**
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Test bench:-

```
module test_bench;
    reg [7:0] data_in;
    reg [2:0] shift_amount;
    reg shift_left;
    wire [7:0] logical_shift_left;
    wire [7:0] logical_shift_right;
    wire [7:0] algebraic_shift_left;
    wire [7:0] algebraic_shift_right;
    wire [7:0] rotate_shift_left;
    wire [7:0] rotate_shift_right;

    logical_shift uut_logical_shift_left (
        .data_in(data_in),
        .shift_amount(shift_amount),
        .shift_left(1'b1),
        .data_out(logical_shift_left)
```



```

);

logical_shift uut_logical_shift_right (
    .data_in(data_in),
    .shift_amount(shift_amount),
    .shift_left(1'b0),
    .data_out(logical_shift_right)
);

algebraic_shift uut_algebraic_shift_left (
    .data_in(data_in),
    .shift_amount(shift_amount),
    .shift_left(1'b1),
    .data_out(algebraic_shift_left)
);

algebraic_shift uut_algebraic_shift_right (
    .data_in(data_in),
    .shift_amount(shift_amount),
    .shift_left(1'b0),
    .data_out(algebraic_shift_right)
);

rotate_shift uut_rotate_shift_left (
    .data_in(data_in),
    .shift_amount(shift_amount),
    .shift_left(1'b1),
    .data_out(rotate_shift_left)
);

rotate_shift uut_rotate_shift_right (
    .data_in(data_in),
    .shift_amount(shift_amount),
    .shift_left(1'b0),
    .data_out(rotate_shift_right)
);

initial begin
    $display("Testing Shift Operations");

    data_in = 8'b11001100;
    shift_amount = 3'b001;
    shift_left = 1'b1;

```

```

#10 $display("Data In: %b", data_in);
$display("Shift Amount: %b", shift_amount);
$display("Logical Shift Left: %b", logical_shift_left);
$display("Logical Shift Right: %b", logical_shift_right);
$display("Algebraic Shift Left: %b", algebraic_shift_left);
$display("Algebraic Shift Right: %b", algebraic_shift_right);
$display("Rotate Shift Left: %b", rotate_shift_left);
$display("Rotate Shift Right: %b", rotate_shift_right);

$finish;
end
endmodule

```

8 ALU

Verilog code:-

```

module alu(
    input [7:0] A,B,
    input [3:0] ALU_Sel,
    output [7:0] ALU_Out,
    output CarryOut
);
reg [7:0] ALU_Result;
wire [8:0] tmp;
assign ALU_Out = ALU_Result;
assign tmp = {1'b0,A} + {1'b0,B};
assign CarryOut = tmp[8];
always @(*)
begin
    case(ALU_Sel)
        4'b0000:
            ALU_Result = A + B ;
        4'b0001:
            ALU_Result = A - B ;
        4'b0010:
            ALU_Result = A * B;
        4'b0011:
            ALU_Result = A/B;
        4'b0100:
            ALU_Result = A<<1;
        4'b0101:
            ALU_Result = A>>1;
        4'b0110:

```

```

        ALU_Result = {A[6:0],A[7]};
4'b0111:
        ALU_Result = {A[0],A[7:1]};
4'b1000:
        ALU_Result = A & B;
4'b1001:
        ALU_Result = A | B;
4'b1010:
        ALU_Result = A ^ B;
4'b1011:
        ALU_Result = ~(A | B);
4'b1100:
        ALU_Result = ~(A & B);
4'b1101:
        ALU_Result = ~(A ^ B);
4'b1110:
        ALU_Result = (A>B)?8'd1:8'd0 ;
4'b1111:
        ALU_Result = (A==B)?8'd1:8'd0 ;
        default: ALU_Result = A + B ;
    endcase
end

```

endmodule

Test bench:-

```

module tb_alu;
reg[7:0] A,B;
reg[3:0] ALU_Sel;

wire[7:0] ALU_Out;
wire CarryOut;

integer i;
alu test_unit(
    A,B,
    ALU_Sel,
    ALU_Out,
    CarryOut
);
initial begin

```

```

A = 8'h0A;
B = 4'h02;
ALU_Sel = 4'h0;

```

```

for (i=0;i<=15;i=i+1)
begin
  ALU_Sel = ALU_Sel + 8'h01;
  #10;
end;

```

```

A = 8'hF6;
B = 8'h0A;


```

```

end
endmodule

```

RTLsymatic:-

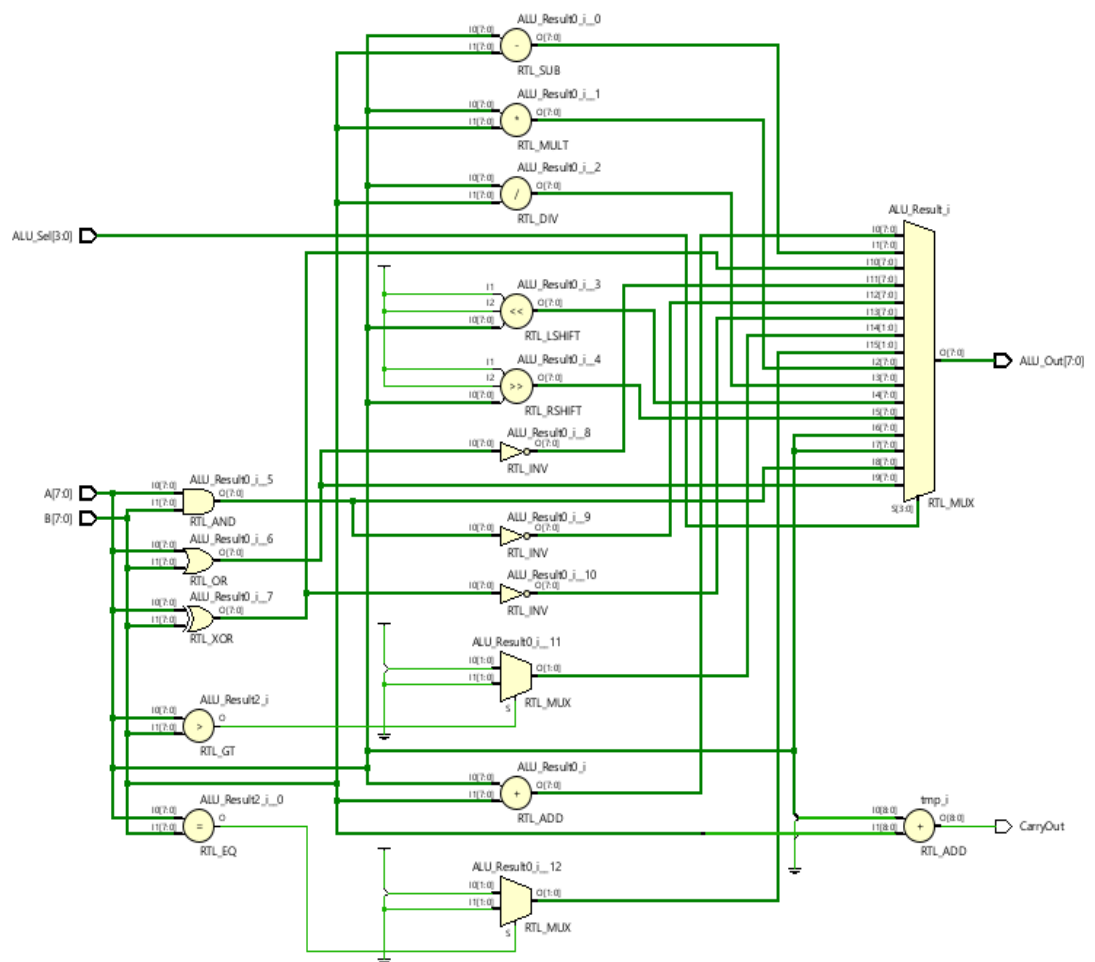

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
CARRY4	34
LUT2	53
LUT3	51
LUT4	26
LUT5	17
LUT6	31
MUXF7	7
IBUF	20
OBUF	9

Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:25 . Memory (MB): peak = 1039.219 ; gain = 23.547


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 7.485 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 71.3°C
Thermal Margin: 53.7°C (8.5 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

9 4-BIT ASYNCHRONOUS DOWN COUNTER

Verilog code:-

```
module down_counter_4bit(
    input wire clk,      // Clock input
    input wire reset,    // Reset input (active low)
    output reg [3:0] count // 4-bit counter output
);

always @(posedge clk or negedge reset) begin
    if (!reset) begin
        count <= 4'b1111; // Reset the counter to its maximum value
    end else begin
        if (count > 4'b0000) begin
```

```

        count <= count - 1; // Decrement the counter
    end
end
end

endmodule

```

Test bench:-

```

module test_bench_down_counter;
    reg clk;
    reg rst;
    wire [3:0] count;

    down_counter_4bit uut (
        .clk(clk),
        .rst(rst),
        .count(count)
    );

    initial begin
        $display("Testing 4-bit Asynchronous Down Counter");

        clk = 0;
        rst = 0;

        #10 rst = 1;
        #10 rst = 0;

        #50;

        $display("Counter Value: %b", count);

        #100;

        $display("Counter Value: %b", count);

        $finish;
    end


    always begin
        #5 clk = ~clk;
    end

```


Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 16.203 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 55.5°C
Thermal Margin: 29.5°C (15.5 W)
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

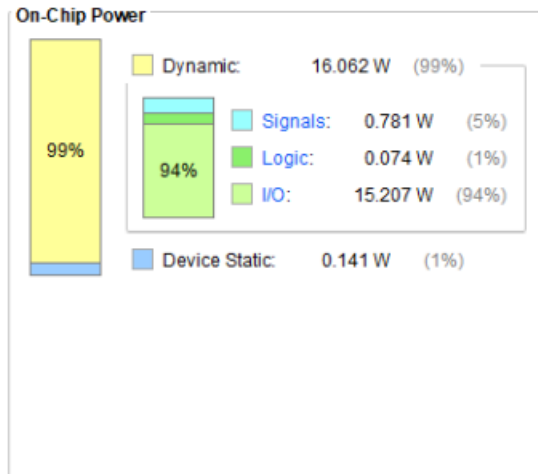[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



10 MOD-N UPDOWN COUNTER

Verilog code:-

```
module up_down_counter (
    input wire clk,
    input wire rst,
    input wire up,
    output wire [3:0] count
);

    reg [3:0] count_reg;

    always @(posedge clk or posedge rst) begin
        if (rst) begin
            count_reg <= 4'b0000;
        end else if (up) begin

            if (count_reg == 4'b0111)
                count_reg <= 4'b0000;
            else
                count_reg <= count_reg + 1;
        end else begin

            if (count_reg == 4'b0000)
                count_reg <= 4'b0111;
            else
                count_reg <= count_reg - 1;
        end
    end

    assign count = count_reg;
endmodule
```



```
endmodule
```

Testbench:-

```
module test_bench;
```

```
    reg clk;  
    reg rst;  
    reg up;  
    wire [3:0] count;
```

```
    up_down_counter uut (  
        .clk(clk),  
        .rst(rst),  
        .up(up),  
        .count(count)  
    );
```

```
    always begin  
        #5 clk = ~clk;  
    end
```

```
    initial begin
```

```
        clk = 0;  
        rst = 0;  
        up = 1;
```

```
        rst = 1;  
        #10 rst = 0;
```

```
        #50 up = 1;  
        #100 up = 0;  
        #100 up = 1;  
        #100 up = 0;
```

```
        $finish;  
    end
```

```
    always @(posedge clk) begin
```


```

    $display("Count: %b", count);
end

```

endmodule

RTIsymatic:-

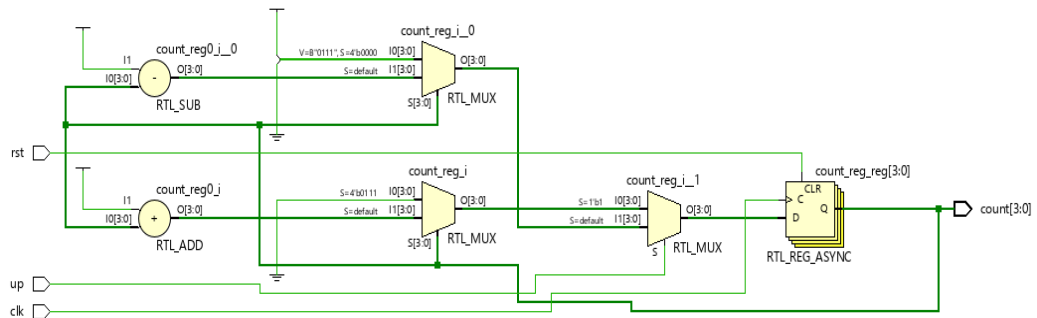

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
| BlackBox name |Instances |
+-----+

```

Report Cell Usage:

```

+-----+
| Cell |Count |
+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:22 ; elapsed = 00:00:24 . Memory (MB): peak = 1019.258 ; gain = 4.250

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.563 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 47.0°C

Thermal Margin: 53.0°C (8.5 W)


Effective θ_{JA} : 6.2°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

11 UNIVERSAL BINARY COUNTER

Verilog code:-

```
module universal_binary_counter (  
    input wire clk,  
    input wire rst,  
    input wire enable,  
    input wire count_up,  
    output wire [3:0] count  
);  
  
    reg [3:0] count_reg;  
  
    always @(posedge clk or posedge rst) begin  
        if (rst) begin  
            count_reg <= 4'b0000;  
        end else if (enable) begin  
            if (count_up) begin  
                count_reg <= count_reg + 4'b0001;  
            end else begin  
                count_reg <= count_reg - 4'b0001;  
            end  
        end  
    end  
  
    assign count = count_reg;  
  
endmodule
```

Test bench:-

```
module tb_universal_binary_counter;  
    reg clk;  
    reg rst;  
    reg enable;  
    reg count_up;  
    wire [3:0] count;  
  
    universal_binary_counter uut (  
        .clk(clk),  
        .rst(rst),  
        .enable(enable),  
        .count_up(count_up),  
        .count(count)  
    );  
endmodule
```

```
always begin
    #5 clk = ~clk;
end
```

```
initial begin
```

```
    clk = 0;
    rst = 0;
    enable = 1;
    count_up = 1;
```


```
    rst = 1;
    #10 rst = 0;
```

```
    $display("Counting Up:");
    for (int i = 0; i < 16; i = i + 1) begin
        #5;
        $display("Count: %b", count);
    end
```

```
    $display("Counting Down:");
    count_up = 0;
    for (int i = 15; i >= 0; i = i - 1) begin
        #5;
        $display("Count: %b", count);
    end
```

```
    $finish;
end
endmodule
```

RTL symatic:-

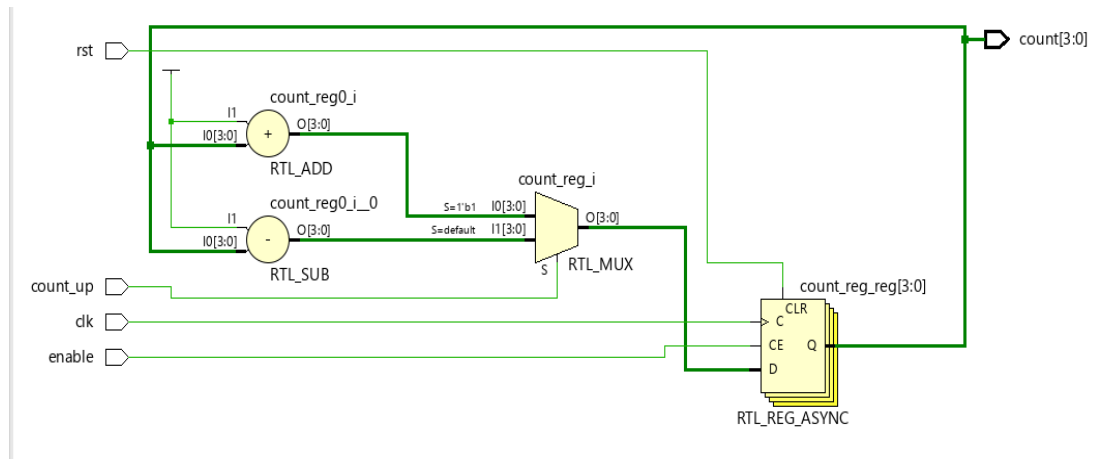

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

	Cell	Count
1	BUFG	1
2	LUT1	1
3	LUT3	1
4	LUT4	1
5	LUT5	1
6	PDCE	4
7	IBUF	4
8	OBUF	4

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:24 . Memory (MB): peak = 1029.250 ; gain = 10.988


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.707 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 47.9°C
 Thermal Margin: 77.1°C (12.3 W)
 Effective θ_{JA} : 6.2°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

12 UNIVERSAL SHIFT REGISTER

Verilog code:-

```

module universal_shift_register (
    input wire clk,
    input wire rst,
    input wire shift_left,
    input wire shift_right,
    input wire enable,
    input wire [3:0] data_in,
    output wire [3:0] data_out
);

    reg [3:0] shift_reg;

    always @(posedge clk or posedge rst) begin
        if (rst) begin
            shift_reg <= 4'b0000;
        end else if (enable) begin
            if (shift_left) begin
                shift_reg <= {shift_reg[2:0], data_in[0]};
            end else if (shift_right) begin
                shift_reg <= {data_in[3], shift_reg[3:1]};
            end
        end
    end

    assign data_out = shift_reg;

endmodule

```

Test bench:-

```

module tb_universal_shift_register;

    reg clk;
    reg rst;
    reg shift_left;
    reg shift_right;
    reg enable;
    wire [3:0] data_in;
    wire [3:0] data_out;

    universal_shift_register uut (
        .clk(clk),
        .rst(rst),
        .shift_left(shift_left),
        .shift_right(shift_right),

```

```
.enable(enable),  
.data_in(data_in),  
.data_out(data_out)  
);
```

```
always begin  
    #5 clk = ~clk;  
end
```

```
initial begin
```

```
    clk = 0;  
    rst = 0;  
    shift_left = 1;  
    shift_right = 0;  
    enable = 1;  
    data_in = 4'b1101;
```

```
    rst = 1;  
    #10 rst = 0;
```


```
    $display("Left Shift:");  
    for (int i = 0; i < 4; i = i + 1) begin  
        #5;  
        $display("Data Out: %b", data_out);  
        data_in = data_in << 1;  
    end
```

```
    $display("Right Shift:");  
    shift_left = 0;  
    shift_right = 1;  
    data_in = 4'b1101;  
    for (int i = 0; i < 4; i = i + 1) begin  
        #5;  
        $display("Data Out: %b", data_out);  
        data_in = data_in >> 1;  
    end
```

```
    $finish;  
end
```

endmodule

RTIsymatic:-

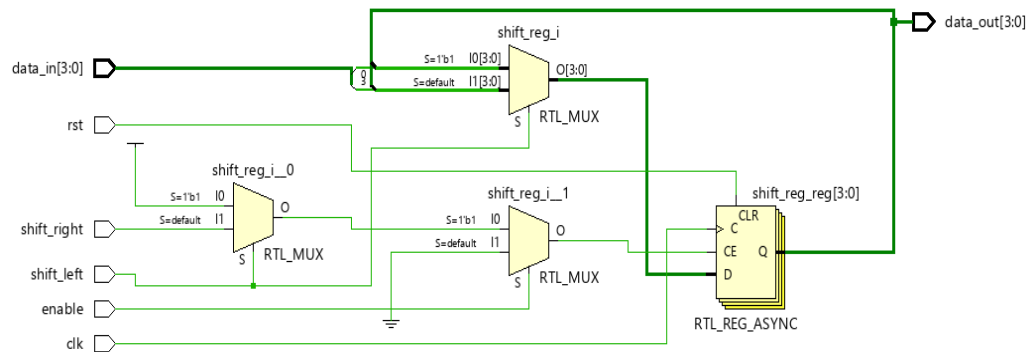

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
```

Report Cell Usage:

```
+-----+
| Cell | Count |
+-----+
|1| |BUFG| | 1|
|2| |LUT3| | 5|
|3| |FDCE| | 4|
|4| |IBUF| | 7|
|5| |OBUF| | 4|
+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:33 ; elapsed = 00:00:44 . Memory (MB): peak = 1032.137 ; gain = 15.234


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.912 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 30.6°C
Thermal Margin: 94.4°C (15.1 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

13 : CN(CHANGE-NO CHANGE FLIPFLOP) USING 2:1 MUX

Verilog code:-

```
module cn_flip_flop (  
    input wire clk,  
    input wire rst,  
    input wire cn,  
    input wire d,  
    output wire q  
);  
  
    reg q_reg;  
    wire mux_out;  
  
    always @(posedge clk or posedge rst) begin  
        if (rst) begin  
            q_reg <= 1'b0;  
        end else if (cn) begin  
            q_reg <= d;  
        end  
    end  
  
    assign mux_out = cn ? d : q_reg;  
  
    assign q = mux_out;  
  
endmodule
```

Test bench:-

```
module tb_cn_flip_flop;  
    reg clk;  
    reg rst;  
    reg cn;  
    reg d;  
    wire q;  
  
    cn_flip_flop uut (  
        .clk(clk),  
        .rst(rst),  
        .cn(cn),  
        .d(d),  
        .q(q)  
    );  
endmodule
```

```
);
```

```
always begin  
    #5 clk = ~clk;  
end
```

```
initial begin
```


```
    clk = 0;  
    rst = 0;  
    cn = 0;  
    d = 0;
```

```
    rst = 1;  
    #10 rst = 0;
```

```
    $display("Clock | CN | D | Q");  
    $display("-----|----|---|---");  
    for (int i = 0; i < 8; i = i + 1) begin  
        d = $random % 2;  
        cn = $random % 2;  
        #5;  
        $display("%4b | %2b | %1b | %1b", clk, cn, d, q);  
    end
```

```
    $finish;  
end  
endmodule
```

RTIsymatic:-

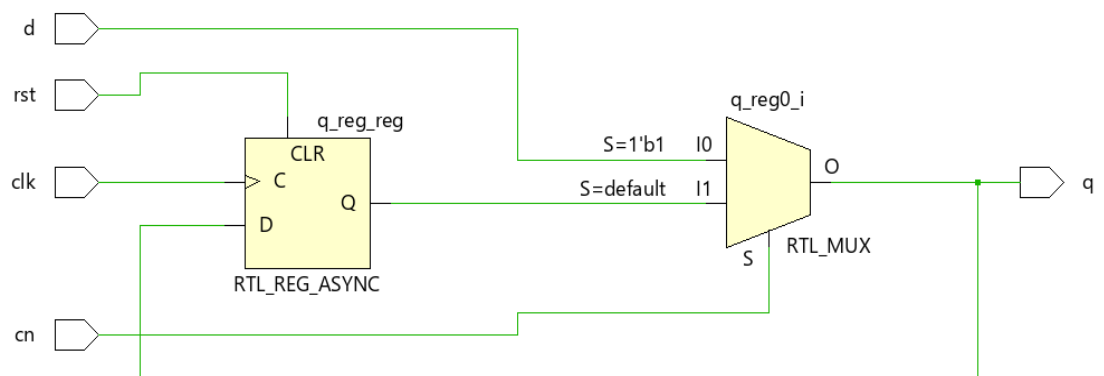

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
| BlackBox name | Instances |
+-----+

```

Report Cell Usage:

```

+-----+
| Cell | Count |
+-----+
| 1 | BUFG | 1 |
| 2 | LUT3 | 1 |
| 3 | FDCE | 1 |
| 4 | IBUF | 4 |
| 5 | OBUF | 1 |
+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:33 ; elapsed = 00:00:40 . Memory (MB): peak = 1033.520 ; gain = 18.836


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.255 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.6°C
 Thermal Margin: 98.4°C (15.7 W)
 Effective θ_{JA} : 6.2°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

14 FREQUENCY DIVIDER BY ODD NUMBERS

Verilog code:-

```
module odd_frequency_divider (
```

```

    input wire clk,
    output wire out
);

reg [2:0] count;

always @(posedge clk) begin

    if (count == 3'b111) begin
        count <= 3'b000;
    end
    else begin
        count <= count + 1;
    end
end

assign out = (count == 3'b100) ? 1'b1 : 1'b0;

endmodule

```

Testbench:-

```

module test_odd_frequency_divider;

    reg clk;
    wire out;

    odd_frequency_divider UUT (
        .clk(clk),
        .out(out)
    );

    always begin
        #5 clk = ~clk;
    end

    initial begin
        clk = 0;
        #10;

        $display("Time=%0t, Clock=%b, Output=%b", $time, clk, out);
        #10;
    end
endmodule

```


```

$finish;
end

endmodule

```

RTIsymatic:-

 

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
LUT1	1
LUT2	1
LUT3	2
FDRE	3
IBUF	1
OBUF	1

Finished Writing Synthesis Report : Time (s): cpu = 00:00:33 ; elapsed = 00:00:38 . Memory (MB): peak = 1042.262 ; gain = 24.605

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.631 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 26.2°C

Thermal Margin: 58.8°C (31.0 W)


Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

15 GREATEST COMMON DIVISOR USING BEHAVIOURAL MODELLING

Verilog code:-

```
module gcd_calculator (  
    input wire [31:0] a,  
    input wire [31:0] b,  
    output wire [31:0] gcd  
);  
  
// Helper function to compute the GCD  
function [31:0] compute_gcd;  
    input [31:0] x, y;  
    begin  
        if (y == 0) begin  
            compute_gcd = x;  
        end else begin  
            compute_gcd = compute_gcd(y, x % y);  
        end  
    end  
endfunction
```

Test bench:-

```
module test_gcd_calculator;  
  
    reg [31:0] a, b;  
    wire [31:0] gcd;  
  
    gcd_calculator UUT (  
        .a(a),  
        .b(b),  
        .gcd(gcd)  
    );  
  
    initial begin  
  
        a = 48;  
        b = 18;  
        #10;  
  
        $display("GCD(%d, %d) = %d", a, b, gcd);  
    end  
endmodule
```

```

    $finish;
end

endmodule

assign gcd = compute_gcd(a, b);

```

```
endmodule
```

16 GREATEST COMMON DIVISOR VIA FSM

Verilog code:-

```

module gcd_calculator (
    input wire clk,
    input wire rst,
    input wire [31:0] a,
    input wire [31:0] b,
    output wire [31:0] gcd,
    output wire done
);

    parameter IDLE = 2'b00;
    parameter COMPARE = 2'b01;
    parameter SUBTRACT = 2'b10;

    reg [1:0] state, next_state;

    always @(posedge clk or posedge rst) begin
        if (rst) begin
            state <= IDLE;
        end else begin
            state <= next_state;
        end
    end

    always @(*) begin
        case(state)
            IDLE: next_state = COMPARE;
            COMPARE: next_state = (a > b) ? SUBTRACT : COMPARE;
            SUBTRACT: next_state = (b > a) ? COMPARE : SUBTRACT;
            default: next_state = IDLE;
        endcase
    end
end

```

```

reg [31:0] a_reg, b_reg;

always @(posedge clk or posedge rst) begin
    if (rst) begin
        a_reg <= 32'b0;
        b_reg <= 32'b0;
    end else if (state == IDLE) begin
        a_reg <= a;
        b_reg <= b;
    end else if (state == SUBTRACT) begin
        a_reg <= a_reg - b_reg;
    end else if (state == COMPARE) begin
        b_reg <= b_reg - a_reg;
    end
end

assign done = (state == IDLE);
assign gcd = (state == IDLE) ? a_reg : b_reg;

endmodule

```

Test bench:-

```

module test_gcd_calculator;

    reg clk;
    reg rst;
    reg [31:0] a, b;
    wire [31:0] gcd;
    wire done;

    gcd_calculator UUT (
        .clk(clk),
        .rst(rst),
        .a(a),
        .b(b),
        .gcd(gcd),
        .done(done)
    );

    initial begin
        clk = 0;
    end

```



```

rst = 0;
a = 48;
b = 18;
#5 rst = 1;
#5 rst = 0;
#10;

$display("GCD(%d, %d) = %d", a, b, gcd);

```

```

$finish;
end

```


```

always begin
    #2 clk = ~clk;
end

```

```
endmodule
```

Rtl symatic:-

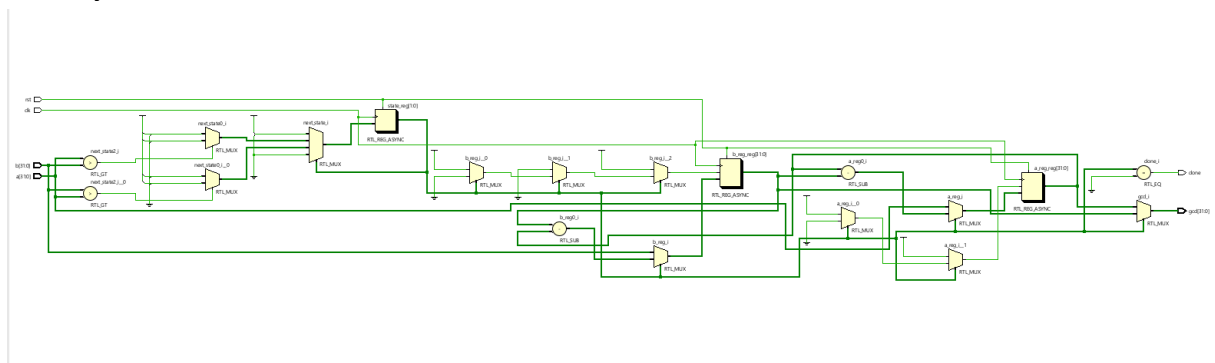

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| CARRY4 | 24|
|3| LUT2 | 66|
|4| LUT3 | 96|
|5| LUT4 | 65|
|6| LUT5 | 1|
|7| FDCE | 66|
|8| FDPE | 1|
|9| IBUF | 66|
|10| OBUF | 33|
+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:00:49 . Memory (MB): peak = 1032.867 ; gain = 13.016

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 7.644 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 72.3°C
Thermal Margin: 52.7°C (8.4 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

17 SINGLE PORT RAM

Verilog code:-

```
module single_port_ram (
    input wire clk,
    input wire we,
    input wire [3:0] addr,
    input wire [7:0] data_in,
    output wire [7:0] data_out
);

reg [7:0] memory [15:0];

always @(posedge clk) begin
```

```

    if (we) begin
        memory[addr] <= data_in;
    end
end

assign data_out = we ? 8'bZZZZ_ZZZZ : memory[addr];

endmodule

```

Testbench:-

```

module test_single_port_ram;

    reg clk;
    reg we;
    reg [3:0] addr;
    reg [7:0] data_in;
    wire [7:0] data_out;

    single_port_ram UUT (
        .clk(clk),
        .we(we),
        .addr(addr),
        .data_in(data_in),
        .data_out(data_out)
    );

    initial begin
        clk = 0;
        we = 1;
        addr = 3'b101;
        data_in = 8'b1101_0011;

        #10 we = 0;

        $display("Read data at address %d: %h", addr, data_out);

        $finish;
    end
end

```

```

always begin
    #5 clk = ~clk;
end


```

```

endmodule

```

RTIsynthesis:-

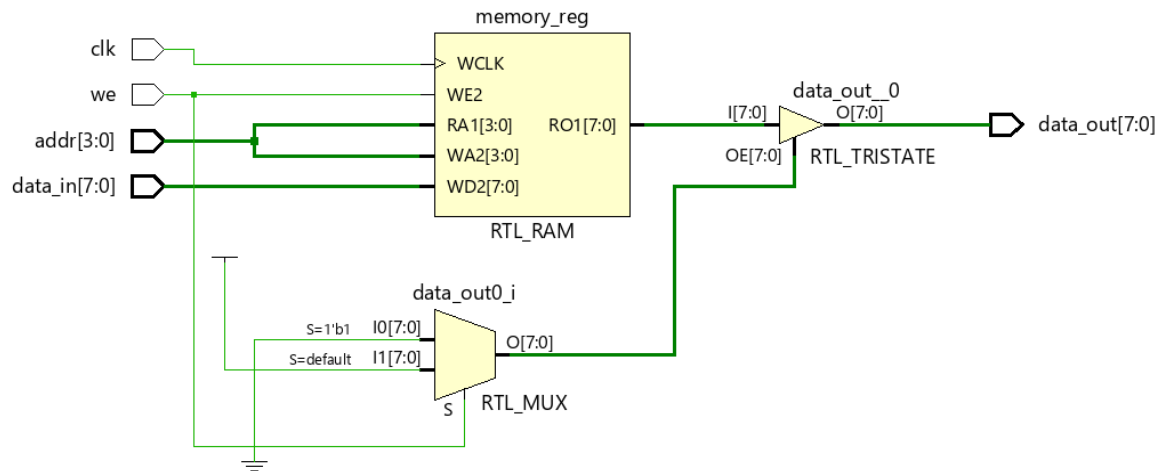

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
RAM16X1S	8
IBUF	14
OBUFT	8

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:25 . Memory (MB): peak = 1034.625 ; gain = 20.000


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.226 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.4°C
 Thermal Margin: 98.6°C (15.8 W)
 Effective θ_{JA} : 6.2°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

18 DUAL PORT RAM

Verilog code:-

```
module dual_port_ram (
  input wire clk,

  input wire we,
  input wire [3:0] addr_w,
  input wire [7:0] data_in,

  input wire re,
  input wire [3:0] addr_r,
  output wire [7:0] data_out
);

reg [7:0] memory [15:0];

always @(posedge clk) begin
  if (we) begin
    memory[addr_w] <= data_in;
  end
end

assign data_out = (re) ? memory[addr_r] : 8'bZZZZ_ZZZZ;

endmodule
```

Test bench:-

```
module test_dual_port_ram;
```

```
reg clk;
reg we;
reg [3:0] addr_w;
reg [7:0] data_in;
reg re;
reg [3:0] addr_r;
wire [7:0] data_out;
```

```
dual_port_ram UUT (
    .clk(clk),
    .we(we),
    .addr_w(addr_w),
    .data_in(data_in),
    .re(re),
    .addr_r(addr_r),
    .data_out(data_out)
);
```

```
initial begin
    clk = 0;
    we = 1;
    addr_w = 3'b101;
    data_in = 8'b1101_0011;
```

```
    #10 we = 0;
```


```
    re = 1;
    addr_r = 3'b101;
    #10;
    $display("Read data at address %d: %h", addr_r, data_out);
```

```
    $finish;
end
```

```
always begin
    #5 clk = ~clk;
end
```

endmodule

RTIsymatic:-

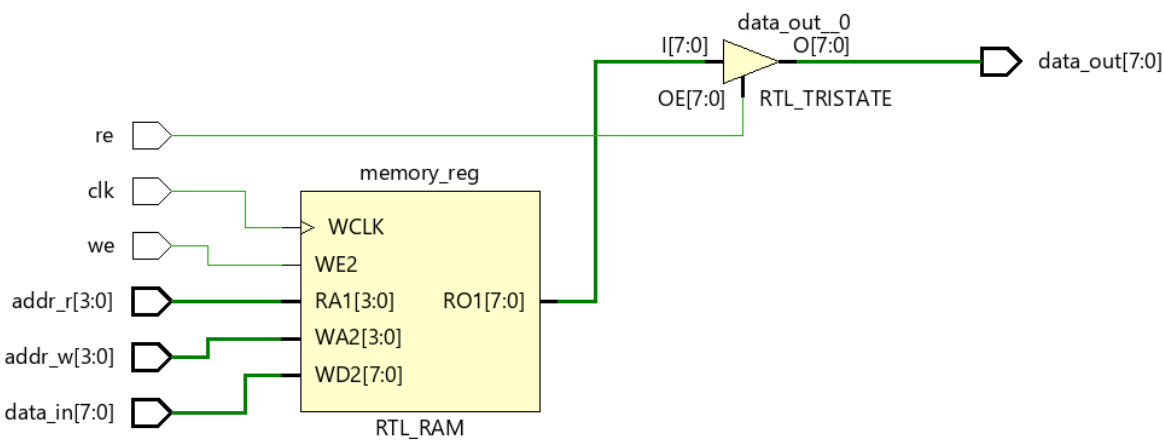

Synthesis report:-

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| BUFG | 1|
|2| LUT1 | 1|
|3| RAM32M | 2|
|4| IBUF | 19|
|5| OBUFT | 8|
+-----+


Finished Writing Synthesis Report : Time (s): cpu = 00:00:16 ; elapsed = 00:00:25 . Memory (MB): peak = 1026.965 ; gain = 7.105
-----
```

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.233 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 32.6°C
Thermal Margin: 92.4°C (14.8 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

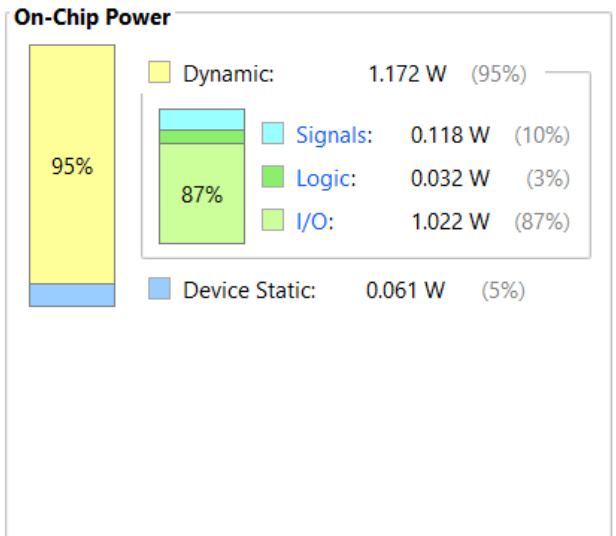[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



19 CLOCK BUFFER

Verilog code:-

```
module clock_buffer (  
    input wire clk_in,  
    output wire clk_out  
);
```

```
    assign clk_out = clk_in;
```

```
endmodule
```

Test bench:-

```
module test_clock_buffer;
```

```
    reg clk_in;  
    wire clk_out;
```

```
    clock_buffer UUT (  
        .clk_in(clk_in),  
        .clk_out(clk_out)  
    );
```

```
    initial begin  
        clk_in = 0;
```

```
    forever begin  
        #5 clk_in = ~clk_in;
```


end

```
$monitor("Time=%0t, Input Clock=%b, Output Clock=%b", $time, clk_in,
clk_out);
```

```
#50;
```

```
$finish;
end
```

endmodule

RTLsymatic:-



Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

	BlackBox name	Instances
1	IBUF	1
2	OBUF	1

Report Cell Usage:

	Cell	Count
1	IBUF	1
2	OBUF	1

Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:25 . Memory (MB): peak = 1018.867 ; gain = 0.000


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.304 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.9°C
Thermal Margin: 98.1°C (15.7 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

20 SYNCHRONOUS FIFO

Verilog code:-

```
module fifo(  
    input wire clk,  
    input wire rst,  
    input wire wr_en,  
    input wire [7:0] data_in,  
    output wire [7:0] data_out,  
    output wire rd_empty,  
    output wire wr_full  
);  
  
parameter DEPTH = 4;  
parameter WIDTH = 8;  
  
reg [WIDTH-1:0] memory [0:DEPTH-1];  
reg [2:0] wr_ptr, rd_ptr;  
reg [3:0] count;  
  
assign data_out = (count == 0) ? 8'b0 : memory[rd_ptr];  
  
assign rd_empty = (count == 0);  
assign wr_full = (count == DEPTH);  
  
always @(posedge clk or posedge rst) begin  
    if (rst) begin  
        wr_ptr <= 3'b0;  
        rd_ptr <= 3'b0;  
    end  
end
```

```

        count <= 0;
    end
    else if (wr_en && !wr_full) begin
        memory[wr_ptr] <= data_in;
        wr_ptr <= wr_ptr + 1;
        count <= count + 1;
    end
    else if (!rd_empty) begin
        rd_ptr <= rd_ptr + 1;
        count <= count - 1;
    end
end
end

```

```
endmodule
```

Testbench:-

```

module tb_fifo();

    reg clk;
    reg rst;
    reg wr_en;
    reg [7:0] data_in;
    wire [7:0] data_out;
    wire rd_empty;
    wire wr_full;

    fifo my_fifo (
        .clk(clk),
        .rst(rst),
        .wr_en(wr_en),
        .data_in(data_in),
        .data_out(data_out),
        .rd_empty(rd_empty),
        .wr_full(wr_full)
    );

    initial begin
        clk = 0;
        rst = 1;
        wr_en = 0;
        data_in = 8'h00;

        #10 rst = 0;
        #10 wr_en = 1;
    end
endmodule

```

```

data_in = 8'hAA;
#10 data_in = 8'h55;
#10 wr_en = 0;
#10 wr_en = 1;
data_in = 8'h33;
#10 data_in = 8'hFF;
#10 wr_en = 0;
#20 $finish;
end

```


```

always begin
#5 clk = ~clk;
end

```

endmodule

RTIsymatic:-

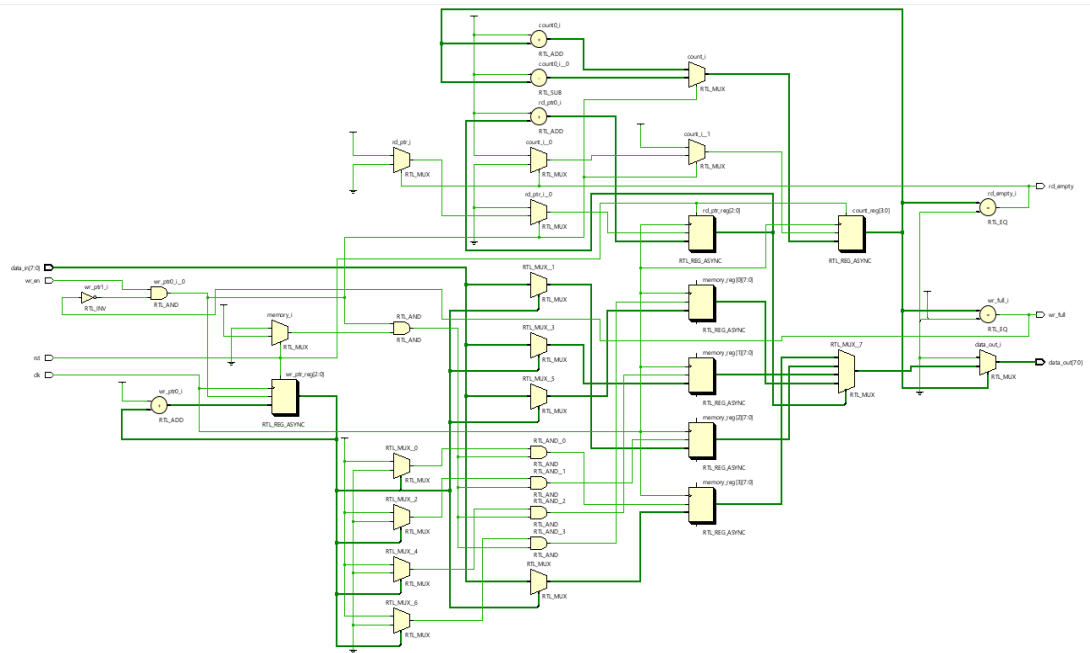

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| |BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+
| |Cell |Count |
+-----+
|1| |BUFG |    1|
|2| |LUT1 |    1|
|3| |LUT3 |    1|
|4| |LUT4 |    7|
|5| |LUT5 |   13|
|6| |LUT6 |   10|
|7| |FDCE |    8|
|8| |FDRE |   32|
|9| |IBUF |   11|
|10| |OBUF |   10|
+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:21 ; elapsed = 00:00:25 . Memory (MB): peak = 1041.223 ; gain = 34.371

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: **6.352 W**
Design Power Budget: **Not Specified**
Power Budget Margin: **N/A**
Junction Temperature: **64.3°C**
Thermal Margin: 35.7°C (5.7 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: **Low**
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

21 PRIORITY ENCODER

Verilog code:-

```
module priority_encoder_4_to_2(
    input wire [3:0] inputs,
    output wire [1:0] encoded
);

assign encoded = (inputs[3]) ? 2'b11 :
                 (inputs[2]) ? 2'b10 :
                 (inputs[1]) ? 2'b01 :
                 2'b00;
```

Test bench:-

```
module tb_priority_encoder_4_to_2();
```

```
reg [3:0] inputs;  
wire [1:0] encoded;
```

```
priority_encoder_4_to_2 my_encoder (
    .inputs(inputs),
    .encoded(encoded)
);
```


```
initial begin
    $display("Testing 4-to-2 Priority Encoder");
    $display("Input (HEX)\tOutput (BIN)");
    $monitor("%h\t\t%b", inputs, encoded);
```

```
for (inputs = 0; inputs < 16; inputs = inputs + 1) begin
    #5;
end
```

```
$finish;  
end
```

endmodule

RTIsynthesis:-

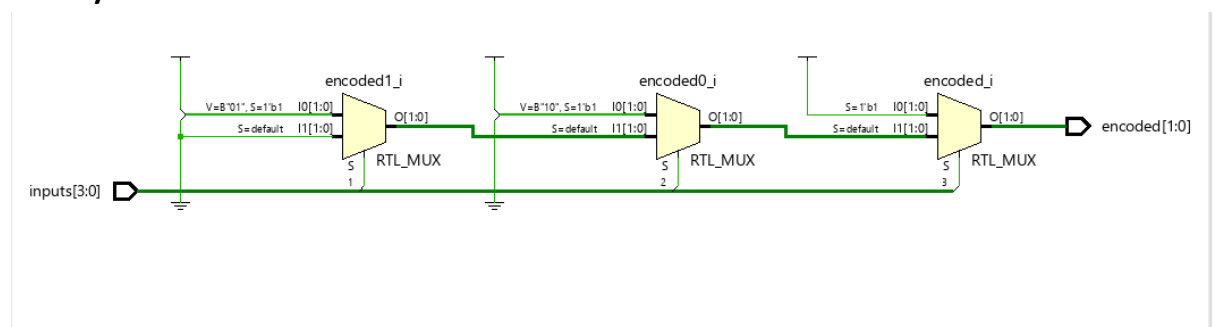

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+
| Cell | Count |
+-----+
| 1 | LUT2 | 1 |
| 2 | LUT3 | 1 |
| 3 | IBUF | 3 |
| 4 | OBUF | 2 |
+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:26 . Memory (MB): peak = 1029.832 ; gain = 12.234


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.59 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 28.6°C
Thermal Margin: 96.4°C (15.4 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

22 SEVEN SEGMENT DISPLAY USING ROM

Verilog code:-

```
module seven_segment_display(  
    input wire [3:0] digit_select,  
    output wire [6:0] segment  
);
```

```
    reg [6:0] rom [0:9];
```

```
initial begin
```

```
    rom[0] = 7'b1000000;
```

```
    rom[1] = 7'b1111001;
```

```
    rom[2] = 7'b0100100;
```

```

rom[3] = 7'b0110000;
rom[4] = 7'b0011001;
rom[5] = 7'b0010010;
rom[6] = 7'b0000010;
rom[7] = 7'b1111000;
rom[8] = 7'b0000000;
rom[9] = 7'b0010000;
end

assign segment = rom[digit_select];

endmodule

```

Testbench:-

```

module tb_seven_segment_display();

reg [3:0] digit_select;
wire [6:0] segment;

seven_segment_display my_display (
    .digit_select(digit_select),
    .segment(segment)
);

initial begin
    $display("Testing Seven-Segment Display");
    $display("Digit\tSegment Pattern (BIN)");


    for (digit_select = 0; digit_select < 10; digit_select = digit_select + 1) begin
        #5;
        end

    $finish;
end

endmodule

```

RTIsymatic:-

 

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
| BlackBox name | Instances |
+-----+
  
```

Report Cell Usage:

```

+-----+
| Cell | Count |
+-----+
| 1 | LUT4 | 7 |
| 2 | IBUF | 4 |
| 3 | OBUF | 7 |
+-----+
  
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:00:44 . Memory (MB): peak = 1032.320 ; gain = 0.000


Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.673 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 35.3°C
 Thermal Margin: 89.7°C (14.3 W)
 Effective θ_{JA} : 6.2°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

23 SERIAL ADDER

Verilog code:-

```

module serial_adder(
    input wire clk,
    input wire rst,
    input wire [3:0] A,
    input wire [3:0] B,
    output wire [3:0] sum
);

reg [3:0] carry;
reg [3:0] temp_sum;

always @(posedge clk or posedge rst) begin
    if (rst) begin
        carry <= 4'b0;
        temp_sum <= 4'b0;
    end
    else begin
        {carry[0], temp_sum[0]} <= A[0] + B[0] + carry[0];
        {carry[1], temp_sum[1]} <= A[1] + B[1] + carry[1];
        {carry[2], temp_sum[2]} <= A[2] + B[2] + carry[2];
        {carry[3], temp_sum[3]} <= A[3] + B[3] + carry[3];
    end
end

assign sum = temp_sum;

endmodule

```

Test bench:-

```

module tb_serial_adder();

reg clk;
reg rst;
reg [3:0] A;
reg [3:0] B;
wire [3:0] sum;

serial_adder my_adder (
    .clk(clk),
    .rst(rst),
    .A(A),
    .B(B),
    .sum(sum)
);

```


Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name |Instances |
+-----+
```

Report Cell Usage:

```
+-----+
| Cell |Count |
+-----+
|1| |BUFG | 1|
|2| |LUT3 | 8|
|3| |FDCE | 8|
|4| |IBUF | 10|
|5| |OBUF | 4|
+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:00:46 . Memory (MB): peak = 1026.422 ; gain = 10.727

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 2.112 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 38.1°C
Thermal Margin: 86.9°C (13.9 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

24 FIXED PRIORITY ARBITER

Verilog code:-

```
module fixed_priority_arbiter(  
    input wire [3:0] requests,  
    output wire [3:0] grant  
);  
  
    assign grant = (requests == 4'b0001) ? 4'b0001 :  
                   (requests == 4'b0010) ? 4'b0010 :  
                   (requests == 4'b0100) ? 4'b0100 :  
                   4'b1000;
```

Endmodule

Test bench:-

```
module tb_fixed_priority_arbiter();
```

```
reg [3:0] requests;
wire [3:0] grant;

fixed_priority_arbiter my_arbiter (
    .requests(requests),
    .grant(grant)
);

initial begin
    $display("Testing Fixed-Priority Arbiter");
    $display("Requests (BIN)\tGrant (BIN)");
    $monitor("%b\t\t\t\b", requests, grant);

    requests = 4'b0001;
    #10 requests = 4'b0000;

    requests = 4'b0010;
    #10 requests = 4'b0000;

    requests = 4'b0100;
    #10 requests = 4'b0000;

    requests = 4'b1000;
    #10 requests = 4'b0000;


    requests = 4'b0011;
    #10 requests = 4'b0000;

    requests = 4'b1100;
    #10 requests = 4'b0000;

    $finish;
end

endmodule
```

RTIsynthesis:-

 

Synthesis report:-

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | LUT4 | 4 |
| 2 | IBUF | 4 |
| 3 | OBUF | 4 |
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:00:50 . Memory (MB): peak = 1032.109 ; gain = 16.793
-----
```

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.68 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	29.2°C
Thermal Margin:	95.8°C (15.3 W)
Effective θ_{JA} :	6.2°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.620 W	(91%)
Device Static:	0.061 W	(9%)
Signals:	0.020 W	(3%)
Logic:	0.011 W	(2%)
I/O:	0.589 W	(95%)

25 ROUND ROBIN ARBITER

Verilog code:-

```

module round_robin_arbiter(
    input wire clk,
    input wire rst,
    input wire [3:0] requests,
    output wire [3:0] grant
);

    reg [1:0] round_robin_pointer;

    always @(posedge clk or posedge rst) begin
        if (rst) begin
            round_robin_pointer <= 2'b00;
        end
        else begin
            if (requests == 4'b0000) begin
                round_robin_pointer <= 2'b00; // No requests, reset pointer
            end
            else begin
                // Round-robin logic
                round_robin_pointer <= round_robin_pointer + 1;
                if (round_robin_pointer == 2'b11) begin
                    round_robin_pointer <= 2'b00; // Wrap around to the beginning
                end
            end
        end
    end

    assign grant = (round_robin_pointer == 2'b00) ? requests :
        (round_robin_pointer == 2'b01) ? requests >> 1 :
        (round_robin_pointer == 2'b10) ? requests >> 2 :
        requests >> 3;

endmodule

```

Test bench:-

```

module tb_round_robin_arbiter();

    reg clk;
    reg rst;
    reg [3:0] requests;
    wire [3:0] grant;

```

```
round_robin_arbiter my_arbiter (
.clk(clk),
.rst(rst),
.requests(requests),
.grant(grant)
);

initial begin
$display("Testing Round-Robin Arbiter");
$display("Requests (BIN)\tGrant (BIN)");
$monitor("%b\t\t\t\b", requests, grant);

rst = 1;
requests = 4'b0001;
#5 rst = 0;
#5;

rst = 1;
requests = 4'b0010;
#5 rst = 0;
#5;

rst = 1;
requests = 4'b0100;
#5 rst = 0;
#5;

rst = 1;
requests = 4'b1000;
#5 rst = 0;
#5;


rst = 1;
requests = 4'b1111;
#5 rst = 0;
#5;

$finish;
end
```


always begin
#5 clk = ~clk;
end

endmodule

RTIsymatic:-

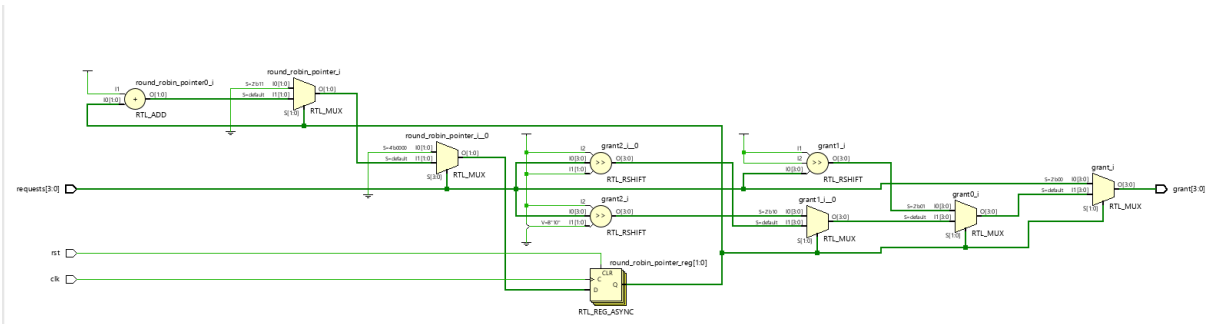

Synthesis report:-

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| |BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| |Cell |Count |
+-----+
|1| |BUFG | 1|
|2| |LUT3 | 1|
|3| |LUT4 | 1|
|4| |LUT5 | 2|
|5| |LUT6 | 2|
|6| |FDCE | 2|
|7| |IBUF | 6|
|8| |OBUF | 4|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:01:00 . Memory (MB): peak = 1032.254 ; gain = 14.828
-----
```

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.327 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 45.6°C
Thermal Margin: 79.4°C (12.7 W)
Effective θ_{JA} : 6.2°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

