

**Name:-Ishan Thakkar**

**ID NO:-21EL032**

**Division:-04**

**Year:-2023-24**

**Subject:-Digital system Desgin (3EL42)**

**Branch:-Electronics**

Q1 clock divider

Verilogcode:-

```
input clock_in;
```

```
output reg clock_out;
```

```
reg[27:0] counter=28'd0;
```

```
parameter DIVISOR = 28'd2;
```

```
always @(posedge clock_in)
```

```
begin
```

```
    counter <= counter + 28'd1;
```

```
    if(counter>=(DIVISOR-1))
```

```
        counter <= 28'd0;
```

```
    clock_out <= (counter<DIVISOR/2)?1'b1:1'b0;
```

```
end
```

```
endmodule
```

testbench:-

```
timescale 1ns / 1ps
```

```
module tb_clock_divider;
```

```
  reg clock_in;
```

```
  wire clock_out;
```

```
  Clock_divider uut (
```

```
    .clock_in(clock_in),
```

```
    .clock_out(clock_out)
```

```
  );
```

```
  initial begin
```


```
    clock_in = 0;
```

```
    forever #10 clock_in = ~clock_in;
```

```
  end
```

```
endmodule
```

RTIsymetic:-

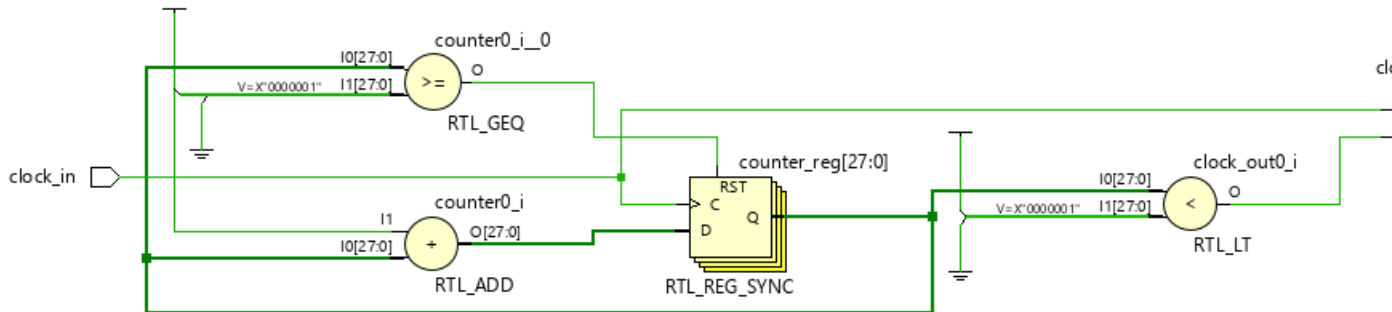

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
| |BlackBox name |Instances |
+-----+
+-----+

```

Report Cell Usage:

```

+-----+
| |Cell |Count |
+-----+
|1 |BUFG |1|
|2 |CARRY4 |7|
|3 |LUT1 |1|
|4 |LUT4 |1|
|5 |LUT5 |2|
|6 |LUT6 |8|
|7 |FDRE |29|
|8 |IBUF |1|
|9 |OBUF |1|
+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:31 ; elapsed = 00:00:37 . Memory (MB):

## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.092 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.6°C


Thermal Margin: 74.4°C (12.0 W)

Effective  $\theta_{JA}$ : 6.2°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

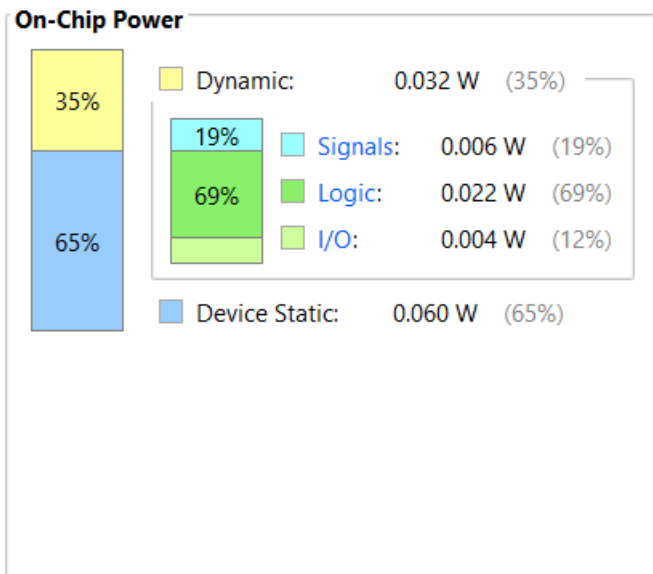[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



## Q2 Johnson counter

Verilog code:-

```
module johnson_counter( out,reset,clk);
```

```
input clk,reset;
```

```
output [3:0] out;
```

```
reg [3:0] q;
```

```
always @(posedge clk)
```

```
begin
```

```
if(reset)
    q=4'd0;
else
    begin
        q[3]<=q[2];
        q[2]<=q[1];
        q[1]<=q[0];
        q[0]<=(~q[3]);
    end
end
```

```
assign out=q;
endmodule
```

Test bench:-

```
module jc_tb;
    reg clk,reset;
    wire [3:0] out;

    johnson_counter dut (.out(out), .reset(reset), .clk(clk));
```

always

    #5 clk =~clk;

initial begin

    reset=1'b1; clk=1'b0;

    #20 reset= 1'b0;

end

initial

    begin


        \$monitor( \$time, " clk=%b, out= %b, reset=%b",  
clk,out,reset);

        #105 \$stop;

    end

endmodule

RTLsymetic:-

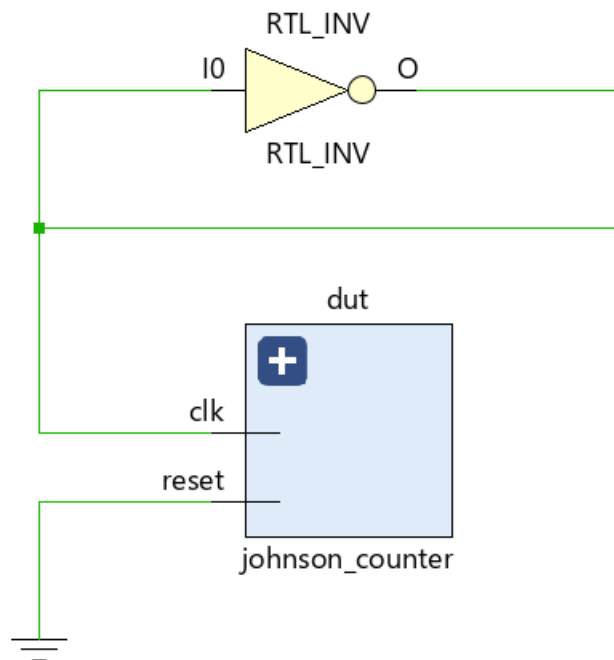

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

```

Report Cell Usage:

```

+-+-----+-----+
| |Cell |Count |
+-+-----+-----+
+-+-----+-----+


```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:31 ; elapsed = 00:00:35 . Memory (MB):
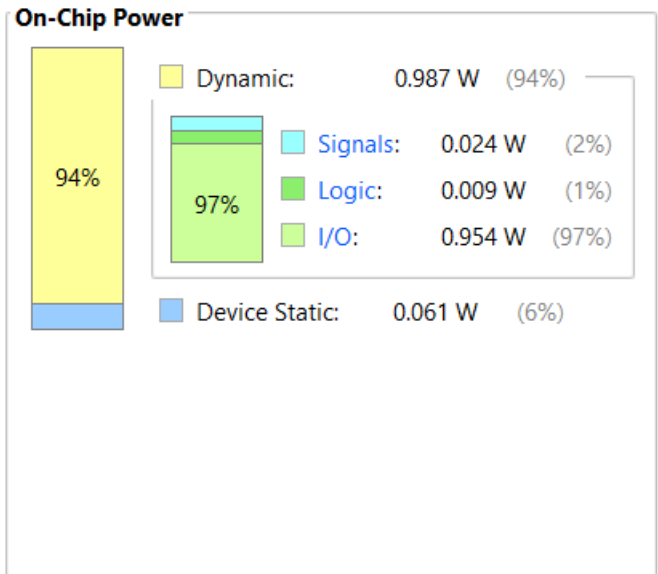
## Powerreport:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 1.048 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 30.5°C  
Thermal Margin: 69.5°C (13.1 W)  
Effective  $\theta_{JA}$ : 5.3°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



### Q3 Ring counter

Verilog code:-

```
module four_bit_ring_counter (  
    input clock,  
    input reset,  
    output [3:0] q  
);  
  
reg[3:0] a;  
  
always @(posedge clock)
```



```
if (reset)
    a = 4'b0001;
```

```
else
    begin
        a <= a<<1;
        a[0]<=a[3];
    end
```

```
assign q = a;
```

```
endmodule
```

Test bench:-

```
timescale 1ns / 1ps
```

```
module stimulus;
```

```
    reg clock;
```

```
    reg reset;
```

```
    wire[3:0] q;
```

```
    four_bit_ring_counter r1 (
        .clock(clock),
```

```
.reset(reset),  
.q(q)  
);
```

```
always #10 clock = ~clock;
```

```
initial begin
```

```
clock = 0;
```

```
reset = 0;
```

```
#5 reset = 1;
```

```
#20 reset = 0;
```

```
#500 $finish;
```

```
end
```


```
initial begin
```

```
$monitor($time, "  
clock=%1b,reset=%1b,q=%4b",clock,reset,q);
```

```
end
```

```
endmodule
```

RTLsymetic:-

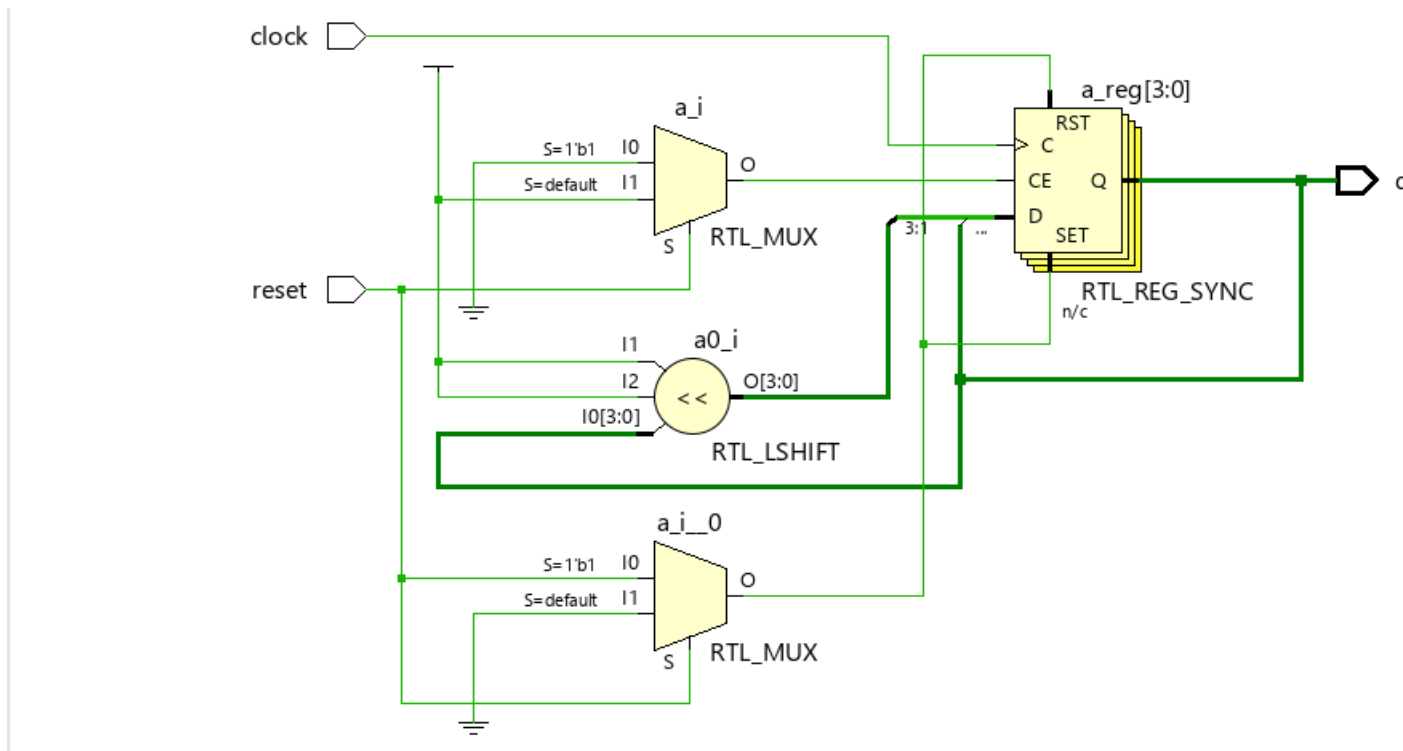

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+
| Cell | Count |
+-----+
| 1 | BUFG | 1 |
| 2 | FDRE | 3 |
| 3 | FDSE | 1 |
| 4 | IBUF | 2 |
| 5 | OBUF | 4 |
+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:24 . Memory (MB):

## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 1.043 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 31.5°C  
Thermal Margin: 68.5°C (11.0 W)  
Effective  $\theta_{JA}$ : 6.2°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## Q4 5 Input Majority circuit

## Verilog code:-

```
module majority_of_five(input [4:0] sw, output led);
```

```
    assign led =    (sw[0] & sw[1] & sw[2]) |  
                    (sw[0] & sw[1] & sw[3]) |  
                    (sw[0] & sw[1] & sw[4]) |  
                    (sw[0] & sw[2] & sw[3]) |  
                    (sw[0] & sw[2] & sw[4]) |  
                    (sw[0] & sw[3] & sw[4]) |  
                    (sw[1] & sw[2] & sw[3]) |  
                    (sw[1] & sw[2] & sw[4]) |  
                    (sw[1] & sw[3] & sw[4]) |  
                    (sw[2] & sw[3] & sw[4]);
```

```
Endmodule
```

Testbench :-

```
`timescale 1ns/ 1ps
```

```
module majority_of_five_tb;
```

```
    reg [4:0] sw;
```

```
    wire led;
```

```
    majority_of_five cut (.sw(sw),.led(led));
```

```
    integer k;
```


```
    initial
```

```

begin
    sw = 0;
    for (k=0; k<32; k=k+1)
        #20 sw = k;
    #20    $finish;
end
endmodule

```

RTLsymetic:-

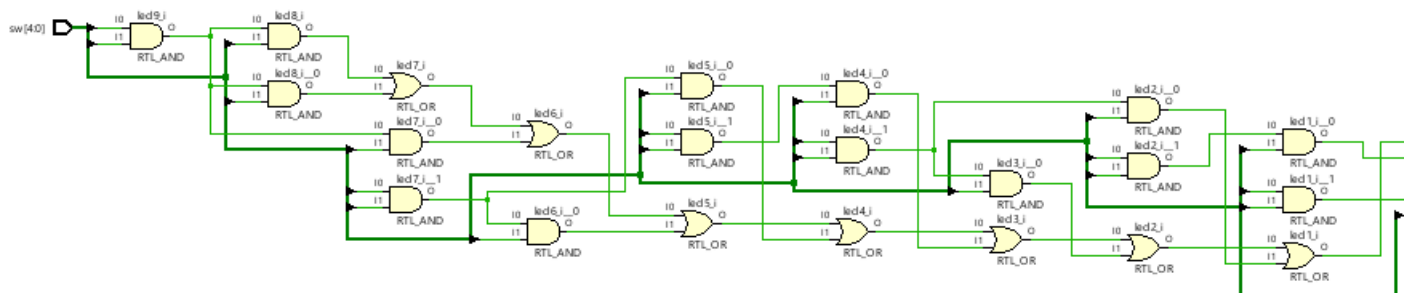

Synthesis report:-

## Start Writing Synthesis Report

### Report BlackBoxes:

BlackBox name	Instances

### Report Cell Usage:

Cell	Count
LUT5	1
IBUF	5
OBUF	1

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:24 . Memory (MB):


## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>0.456 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>27.4°C</b>
Thermal Margin:	72.6°C (13.7 W)
Effective $\theta_{JA}$ :	5.3°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## Q5 Parity Generator

## Verelogs code:-

```
module parity(
```

```
input x,y,z,
```

```
output result);
```

```
xor (result,x,y,z);
```

```
endmodule
```

Testbench:-

```
initial begin
```

```
x = 0;
```

```
y = 0;
```



`z = 0;`

`#100;`

`x = 0;`

`y = 0;`

`z = 1;`

`#100;`

`x = 0;`

`y = 1;`

`z = 0;`

`#100;`

`x = 0;`

`y = 1;`

`z = 1;`

`#100;`

`x = 1;`

`y = 0;`

`z = 0;`

#100;

x = 1;

y = 0;

z = 1;

#100;

x = 1;

y = 1;

z = 0;

#100;

```
x = 1;
```

```
y = 1;
```


```
z = 1;
```

```
#100;
```

```
end
```

```
endmodule
```

RTL symetic:-

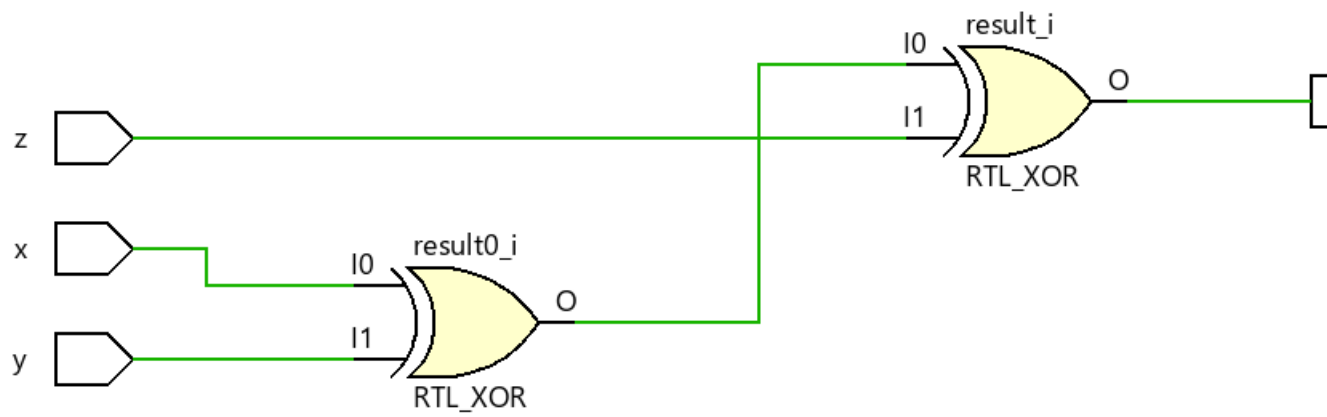

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

++-----+
| |BlackBox name |Instances |
++-----+
++-----+

```

Report Cell Usage:

```

+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |LUT3 |    1|
|2      |IBUF |    3|
|3      |OBUF |    1|
+-----+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:23 . Memory (MB):


## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.633 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 28.3°C  
Thermal Margin: 71.7°C (13.6 W)  
Effective  $\theta_{JA}$ : 5.3°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

Q6 one hot to binary encoding:-

Verilog code:-

```
module BinaryToOneHotEncoder (
```

```
    input [3:0] binary_input,
```

```
    output [7:0] one_hot_output
```

```
);
```

```
    always @(*) begin
```

```
        case (binary_input)
```

```
            4'b0001: one_hot_output = 8'b00000001;
```

```
            4'b0010: one_hot_output = 8'b00000010;
```

```
            4'b0100: one_hot_output = 8'b00000100;
```

```
        4'b1000: one_hot_output = 8'b00001000;
        default: one_hot_output = 8'b00000000;
    endcase
end
```

```
endmodule
```

Testbench:-

```
reg [3:0] binary_input;
wire [7:0] one_hot_output;

BinaryToOneHotEncoder UUT (
    .binary_input(binary_input),
    .one_hot_output(one_hot_output)
);

initial begin
    $display("Testing Binary to One-Hot Encoder");
    binary_input = 4'b0000;
    #10 $display("Input: %b, Output: %b", binary_input,
one_hot_output);
```

```
binary_input = 4'b0001;  
#10 $display("Input: %b, Output: %b", binary_input,  
one_hot_output);
```

```
binary_input = 4'b0010;  
#10 $display("Input: %b, Output: %b", binary_input,  
one_hot_output);
```

```
binary_input = 4'b0100;  
#10 $display("Input: %b, Output: %b", binary_input,  
one_hot_output);
```

```
binary_input = 4'b1000;  
#10 $display("Input: %b, Output: %b", binary_input,  
one_hot_output);
```


```
binary_input = 4'b1010; // Invalid input  
#10 $display("Input: %b, Output: %b", binary_input,  
one_hot_output);
```

```
$finish;  
end
```



endmodule

RTLSynthesis:-

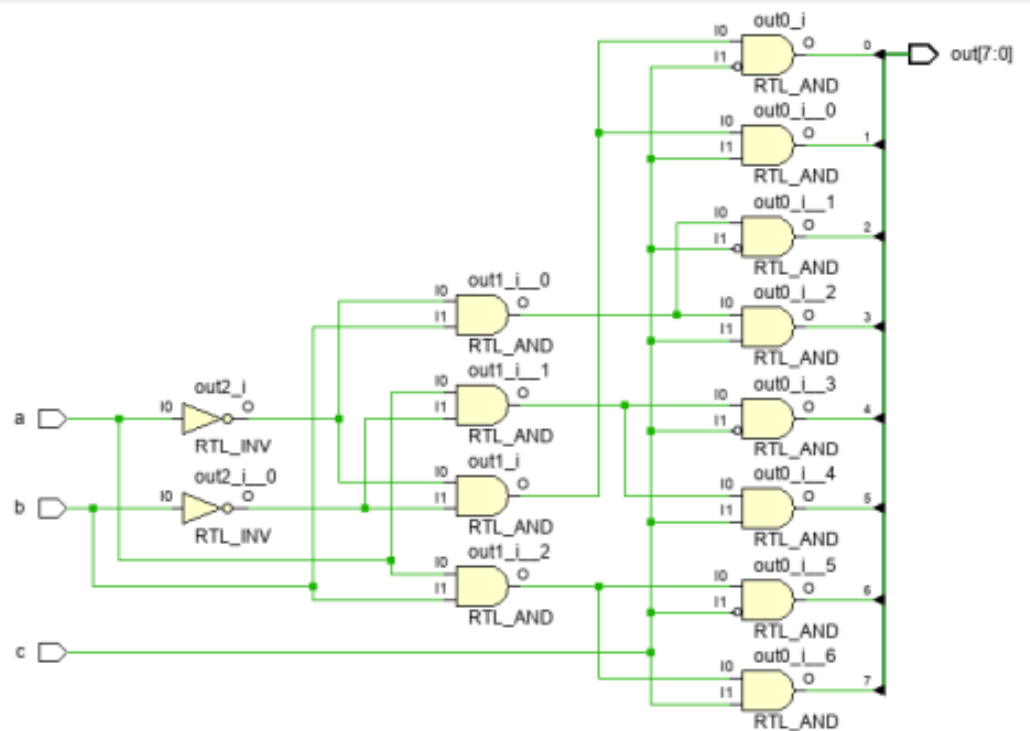

Synthesis report:-

```
-----  
Start Writing Synthesis Report  
-----
```

Report BlackBoxes:

```
+-----+  
| BlackBox name |Instances |  
+-----+  
+-----+
```

Report Cell Usage:

```
+-----+  
| Cell |Count |  
+-----+  
|1     |LUT3 |    8|  
|2     |IBUF |    3|  
|3     |OBUF |    8|  
+-----+
```

Report Instance Areas:

```
+-----+  
| Instance |Module |Cells |  
+-----+  
|1         |top    |    19|  
+-----+
```

```
-----  
Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:30 . Memory (MB): peak = 1019.4  
-----
```

Power report:-


## Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>1.393 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>27.6°C</b>
<b>Thermal Margin:</b>	<b>57.4°C (30.3 W)</b>
<b>Effective <math>\theta_{JA}</math>:</b>	<b>1.9°C/W</b>
<b>Power supplied to off-chip devices:</b>	<b>0 W</b>
<b>Confidence level:</b>	<b>Low</b>

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

## On-Chip Power

 

## Q7 .4-BIT BCD SYNCHRONOUS COUNTER

Verilog code:-

```
timescale 1ns / 1ps
```

```
module bcd_counter(input clk, reset, output reg [3:0] q);
```

```
reg [3:0] t;
```

```
always @ (posedge clk) begin
```

```
    if (reset)
```

```
    begin
```

```
        t <= 4'b0000;
```

```
        q <= 4'b0000;
```

```
    end
```

```
else
begin
    t <= t + 1;
    if (t == 4'b1001)
    begin
        t <= 4'b0000;
    end
    q <= t;
end
end
endmodule
```

Testbench:-


```
module bcd_counter_tb;
reg clk;
reg reset;
wire [3:0] q;

bcd_counter DUT(.clk(clk), .reset(reset), .q(q));
initial begin
    clk = 0;
```

```
    forever #5 clk = ~clk;
end

initial begin
    reset = 1;
    #10 reset = 0;
    $monitor ("T=%0t out=%b", $time, q);
    #150 reset = 1;
    #10 reset = 0;
    #200
    $finish;
end
endmodule
```

RTLsymetic:-

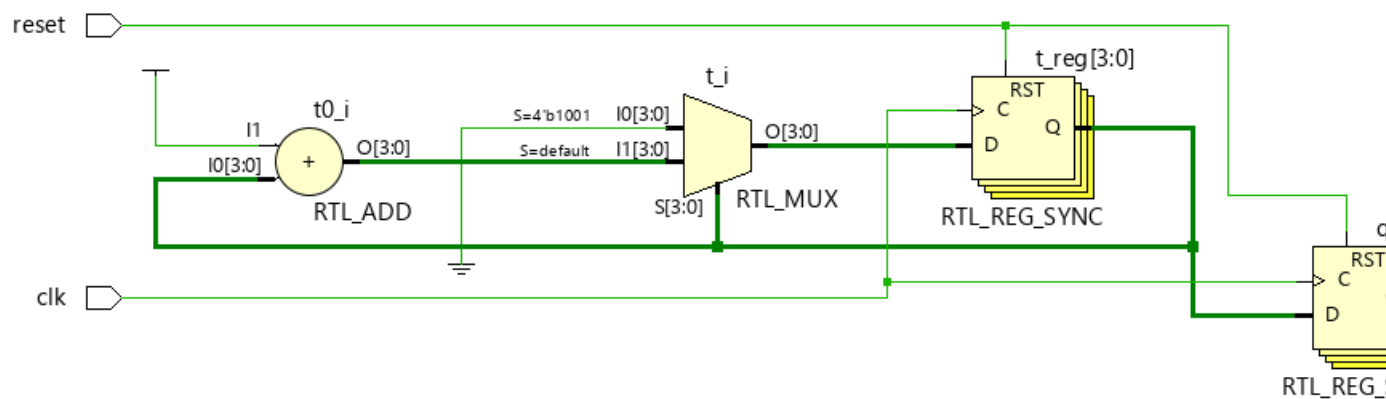

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

++-----+
| |BlackBox name |Instances |
++-----+
++-----+

```

Report Cell Usage:

```

+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |BUFG |    1|
|2      |LUT1 |    1|
|3      |LUT3 |    1|
|4      |LUT4 |    2|
|5      |FDRE |    8|
|6      |IBUF |    2|
|7      |OBUF |    4|
+-----+-----+

```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:19 ; elapsed = 00:00:25 . Memory (MB):

## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** **3.582 W**  
**Design Power Budget:** **Not Specified**  
**Power Budget Margin:** **N/A**  
**Junction Temperature:** **43.9°C**  
Thermal Margin: 56.1°C (10.6 W)  
Effective  $\theta_{JA}$ : 5.3°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: **Low**

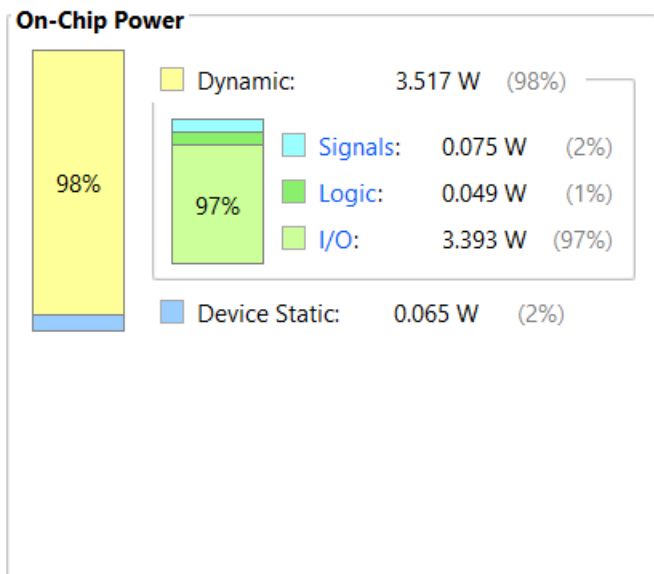[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



## Q8 4-BIT CARRY LOOKAHEAD ADDER

### Verilog code:-

```
module CarryLookAheadAdder(  
    input [3:0]A, B,  
    input Cin,  
    output [3:0] S,  
    output Cout  
);  
    wire [3:0] Ci;
```

```
assign Ci[0] = Cin;
```

```
assign Ci[1] = (A[0] & B[0]) | ((A[0]^B[0]) & Ci[0]);
```

```
assign Ci[2] = (A[1] & B[1]) | ((A[1]^B[1]) & ((A[0] & B[0]) |  
((A[0]^B[0]) & Ci[0])));
```

```
assign Ci[3] = (A[2] & B[2]) | ((A[2]^B[2]) & ((A[1] & B[1]) |  
((A[1]^B[1]) & ((A[0] & B[0]) | ((A[0]^B[0]) & Ci[0])))));
```

```
assign Cout = (A[3] & B[3]) | ((A[3]^B[3]) & ((A[2] & B[2]) |  
((A[2]^B[2]) & ((A[1] & B[1]) | ((A[1]^B[1]) & ((A[0] & B[0]) |  
((A[0]^B[0]) & Ci[0]))))));
```

```
assign S = A^B^Ci;
```

Testbench:-

```
module TB;
```

```
reg [3:0]A, B;
```

```
reg Cin;
```

```
wire [3:0] S;
```

```
wire Cout;
```



```
wire[4:0] add;
```

```
CarryLookAheadAdder cla(A, B, Cin, S, Cout);
```

```
assign add = {Cout, S};
```

```
initial begin
```

```
    $monitor("A = %b: B = %b, Cin = %b --> S = %b, Cout = %b,  
Addition = %0d", A, B, Cin, S, Cout, add);
```

```
    A = 1; B = 0; Cin = 0; #3;
```

```
    A = 2; B = 4; Cin = 1; #3;
```


```
    A = 4'hb; B = 4'h6; Cin = 0; #3;
```

```
    A = 5; B = 3; Cin = 1;
```

```
end
```

```
endmodule
```

RTL symetic:-

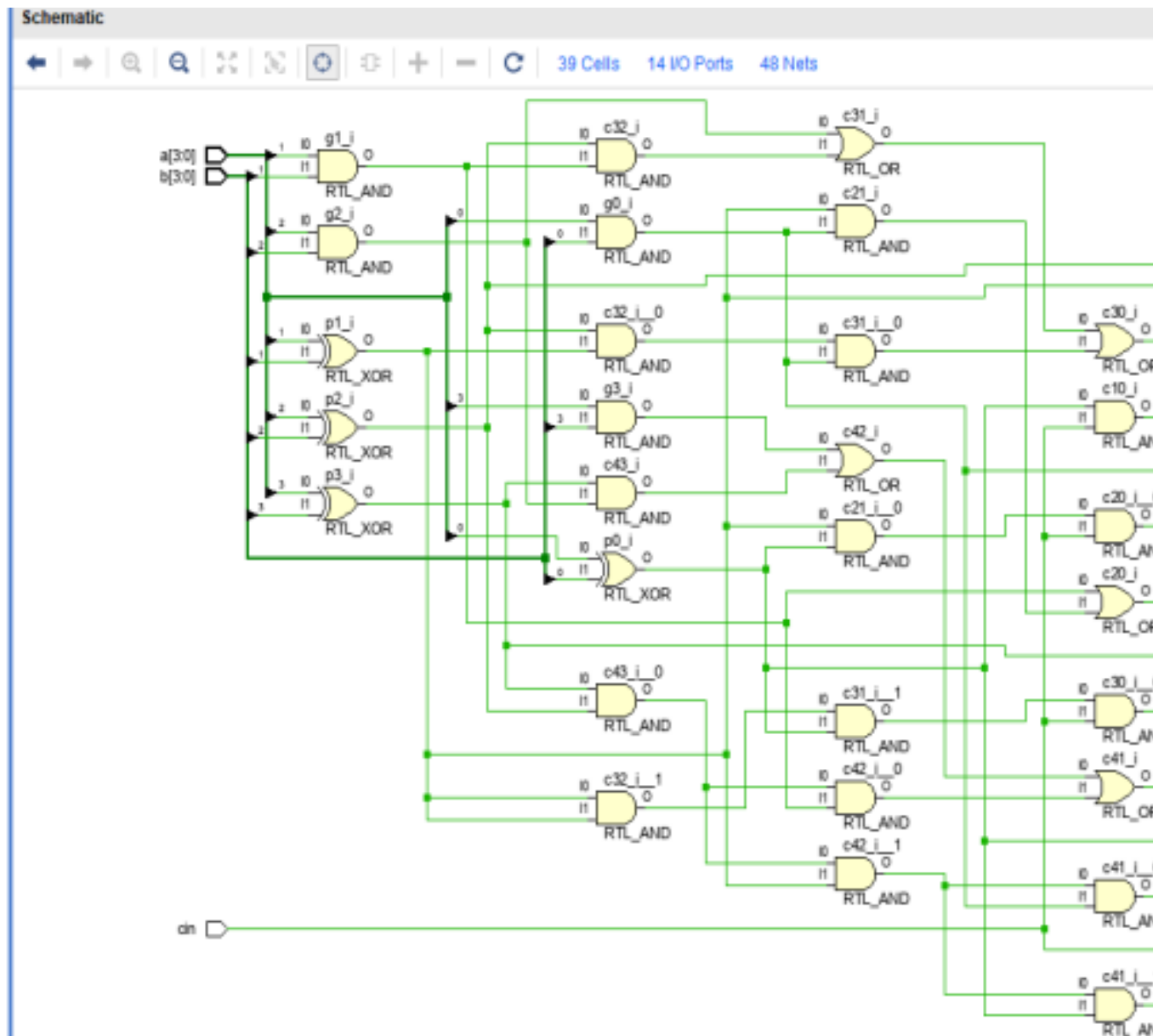

Synthesis report:-

## Start Writing Synthesis Report

---

### Report BlackBoxes:

BlackBox name	Instances

### Report Cell Usage:

	Cell	Count
1	LUT2	1
2	LUT3	1
3	LUT4	1
4	LUT5	4
5	LUT6	2
6	IBUF	9
7	OBUF	5

### Report Instance Areas:

Instance	Module	Cells
1	top	23

---

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:32 . Memory

Power report:-


## Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>3.003 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>30.7°C</b>
<b>Thermal Margin:</b>	<b>54.3°C (28.7 W)</b>
<b>Effective <math>\theta_{JA}</math>:</b>	<b>1.9°C/W</b>
<b>Power supplied to off-chip devices:</b>	<b>0 W</b>
<b>Confidence level:</b>	<b>Low</b>

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

## On-Chip Power

 

Q9 n bit comparator

Verilog code:-

```
module comparator(a,b,eq,lt,gt);
```

```
input [3:0] a,b;
```

```
output reg eq,lt,gt;
```

```
always @(a,b)
```

```
begin
```

```
if (a==b)
```

```
begin
```

```
eq = 1'b1;
```

```
lt = 1'b0;
```

```
gt = 1'b0;
```

```
end
```

```
else if (a>b)
```

```
begin
```

```
eq = 1'b0;
```

```
lt = 1'b0;
```

```
gt = 1'b1;
```

```
end
```

```
else
```

```
begin
```

```
eq = 1'b0;
```

```
lt = 1'b1;
```

```
gt = 1'b0;
```

```
end
```

```
end
```

```
endmodule
```

Testbench:-

```
module comparator(a,b,eq,lt,gt);
```

```
input [3:0] a,b;
```

```
output reg eq,lt,gt;
```

```
always @(a,b)
```

```
begin
```

```
if (a==b)
```

```
begin
```

```
eq = 1'b1;
```

```
lt = 1'b0;
```

```
gt = 1'b0;
```

```
end
```

```
else if (a>b)
```

```
begin
```

```
eq = 1'b0;
```


```
lt = 1'b0;
```

```

gt = 1'b1;
end
else
begin
eq = 1'b0;
lt = 1'b1;
gt = 1'b0;
end
end
endmodule

```

RTLsymetic:-

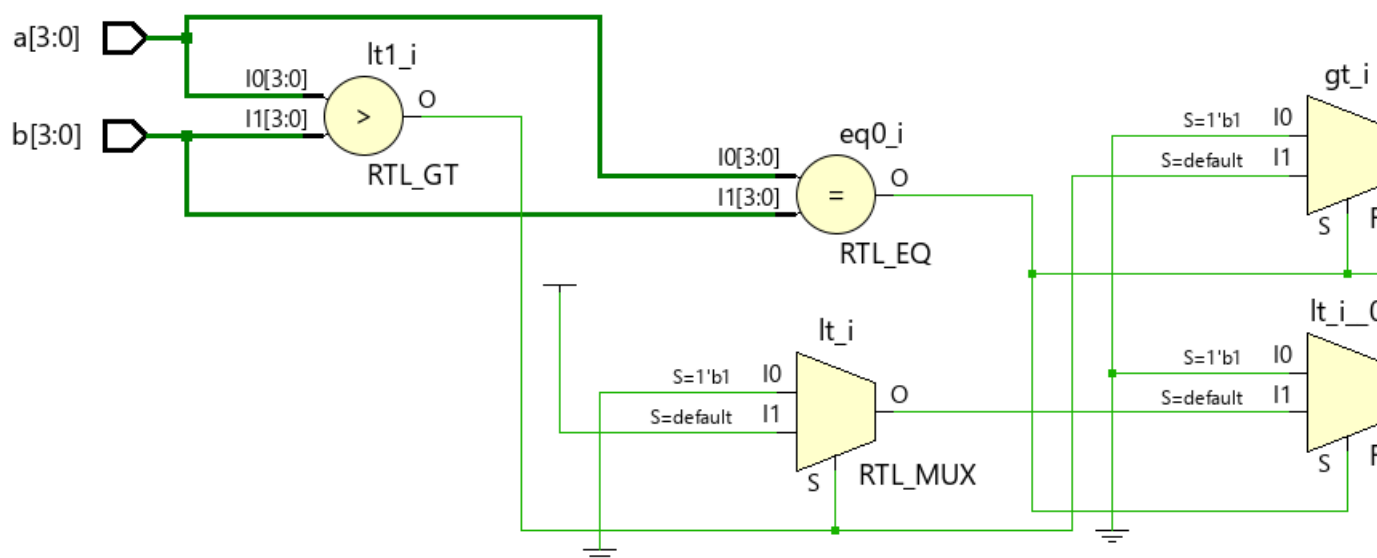

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

	Cell	Count
1	LUT3	1
2	LUT4	2
3	LUT6	2
4	IBUF	8
5	OBUF	3

Finished Writing Synthesis Report : Time (s): cpu = 00:00:31 ; elapsed = 00:00:37 . Memory (MB):


## Power report:-



Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 1.061 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 31.6°C  
 Thermal Margin: 93.4°C (14.9 W)  
 Effective  $\theta_{JA}$ : 6.2°C/W  
 Power supplied to off-chip devices: 0 W  
 Confidence level: Low

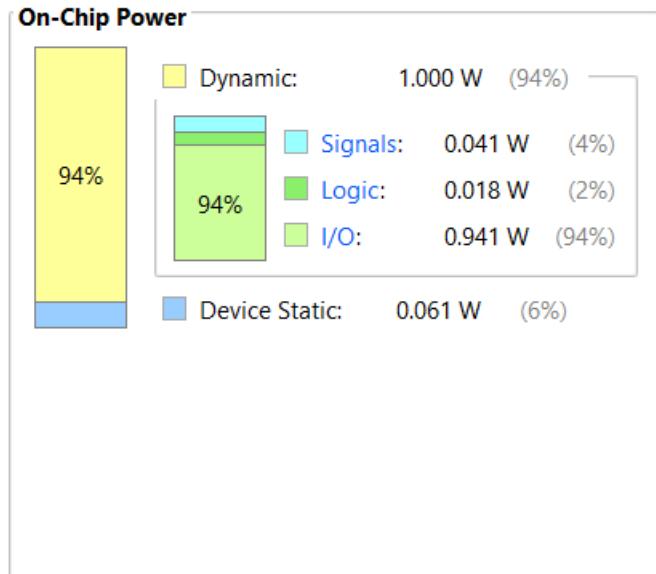[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q10 serial register in serial register out

Verilog code:-

```
timescale 1ns / 1ps
module siso_design(input clk,b,output q);
wire w1,w2,w3;

d_ff dut1(.clk(clk),.d(b),.q(w1),.rst());
d_ff dut2(.clk(clk),.d(w1),.q(w2),.rst());
d_ff dut3(.clk(clk),.d(w2),.q(w3),.rst());
d_ff dut4(.clk(clk),.d(w3),.q(q),.rst());

endmodule

// d flip flop
module d_ff (
  input clk,
```

```
input d,  
input rst,  
output reg q);
```

```
always @(posedge clk)  
begin  
    if (rst)  
        q <= 1'b0;  
    else  
        q <= d;  
end
```

```
endmodule
```

testbench:-

```
// testbench  
module siso_tb();
```

```
reg clk,b;  
wire q;
```

```
siso_design uut(.clk(clk),.b(b),.q(q));
```

```
initial  
begin  
    clk=1'b0;  
    forever #5clk=~clk;  
end
```

```
initial
begin
$monitor("clk=%d,b=%d,q=%d",clk,b,q);
end
```


```
initial
begin
b=1;
#10;
b=1;
#10;
b=1;
#10;
b=0;
```

```
#50;
$finish;
```

```
End
```

```
Endmodule
```

RTLsymetic:-

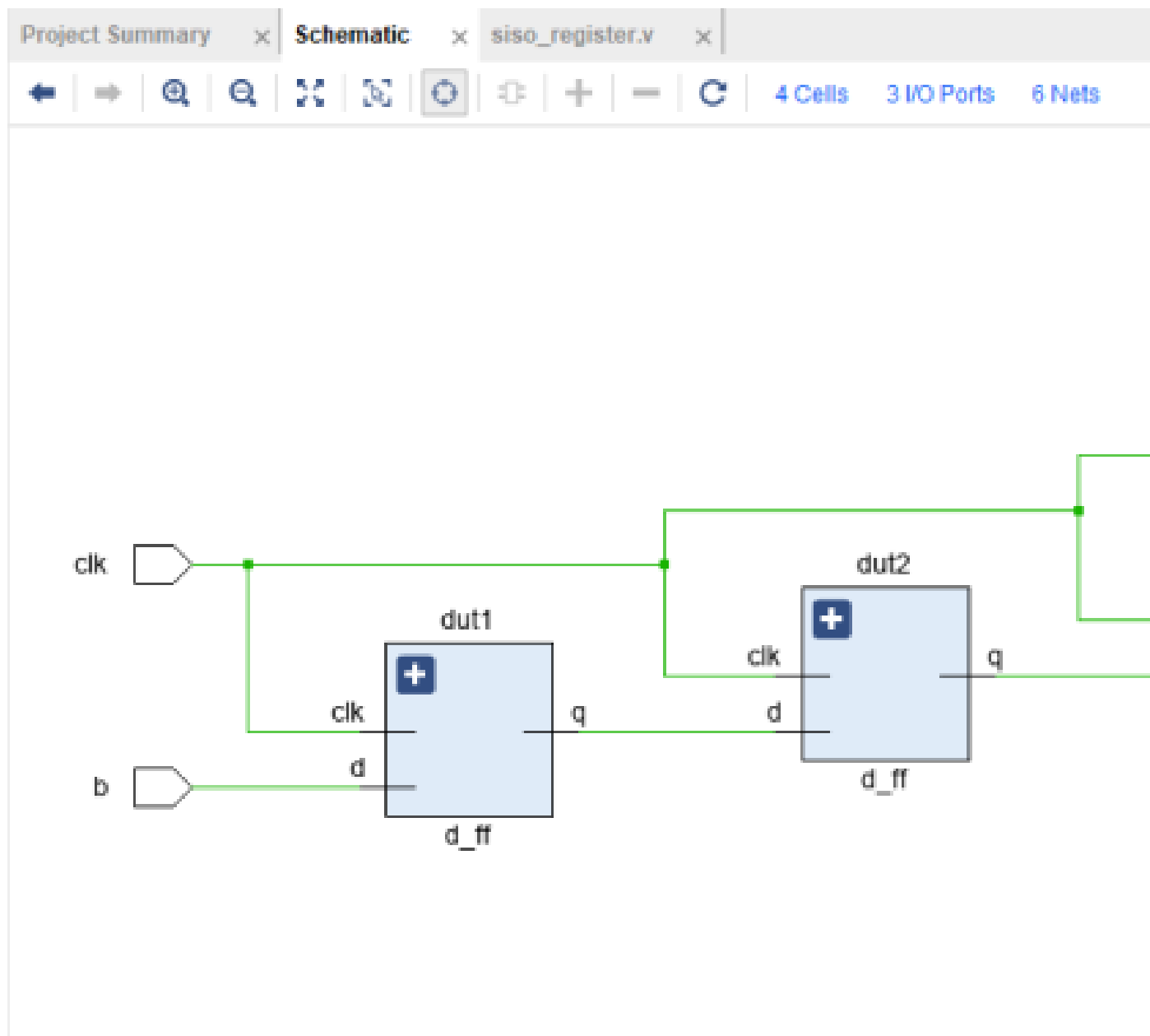

Synthesis report:-

## Start Writing Synthesis Report

---

### Report BlackBoxes:

BlackBox name	Instances

### Report Cell Usage:

	Cell	Count
1	BUFG	1
2	SRL16E	1
3	FDRE	2
4	IBUF	2
5	OBUF	1

### Report Instance Areas:

	Instance	Module	Cells
1	top		7
2	dut1	d_ff	1
3	dut3	d_ff_0	1
4	dut4	d_ff_1	1

---

Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>0.351 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>25.7°C</b>
<b>Thermal Margin:</b>	<b>59.3°C (31.3 W)</b>
<b>Effective <math>\theta_{JA}</math>:</b>	<b>1.9°C/W</b>
<b>Power supplied to off-chip devices:</b>	<b>0 W</b>
<b>Confidence level:</b>	<b>Low</b>

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip P

77%

23%

Q11 Serial in parallel out shift register

Verilog code:-

```
module sipo_shift_register #(parameter N=4) (
```

```
input clk,  
input reset,  
input serial_in,  
output [N-1:0] parallel_out  
);
```

```
reg [N-1:0] shift_register;
```

```
always @(posedge clk or posedge reset) begin  
    if (reset)  
        shift_register <= 0;  
    else  
        shift_register <= {shift_register[N-2:0], serial_in};  
end
```

```
assign parallel_out = shift_register;
```

```
endmodule
```

Testbench:-

```
module testbench_sipo;
```

```
parameter N = 4;  
parameter CLK_PERIOD = 10;
```

```
reg clk;  
reg reset;  
reg serial_in;  
wire [N-1:0] parallel_out;
```

```
sipo_shift_register #(N) uut (  
    .clk(clk),  
    .reset(reset),  
    .serial_in(serial_in),  
    .parallel_out(parallel_out)  
);
```

```
always begin  
    #CLK_PERIOD / 2 clk = ~clk;
```



end

initial begin

  \$display("SIPO Shift Register Testbench");

  clk = 0;

  reset = 1;

  serial\_in = 0;

  #CLK\_PERIOD reset = 0;

  serial\_in = 1;

  #CLK\_PERIOD serial\_in = 0;

  #CLK\_PERIOD serial\_in = 1;

  #CLK\_PERIOD serial\_in = 0;

  reset = 1;

  #CLK\_PERIOD reset = 0;


```
$display("Parallel Out: %b", parallel_out);
```

```
$finish;
```

```
end
```

```
endmodule
```

RTLSynthesis :-

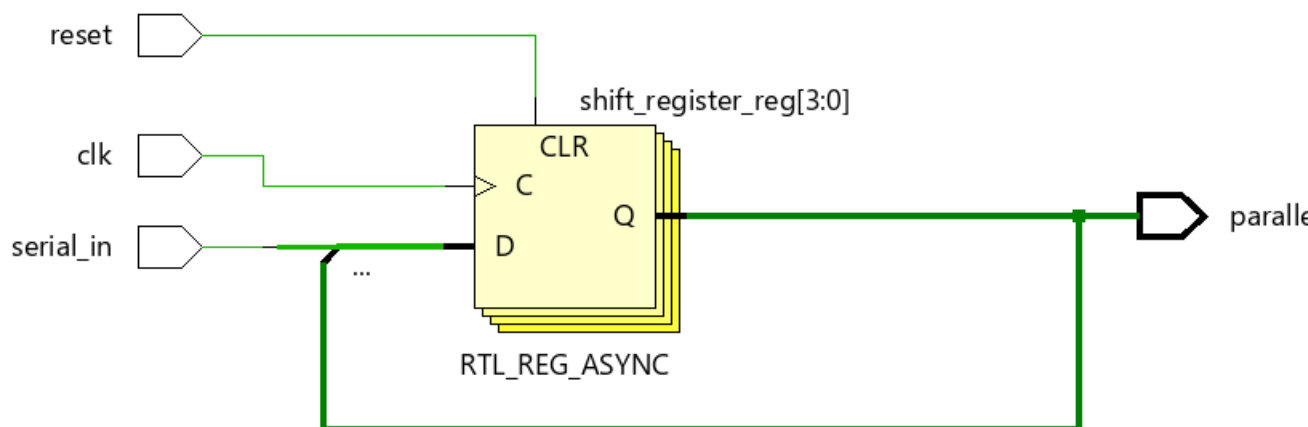

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
FDCE	4
IBUF	3
OBUF	4


Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:00:36 . Memory (MB):

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	1.088 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	27.8°C
Thermal Margin:	72.2°C (27.4 W)
Effective ΘJA:	2.6°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

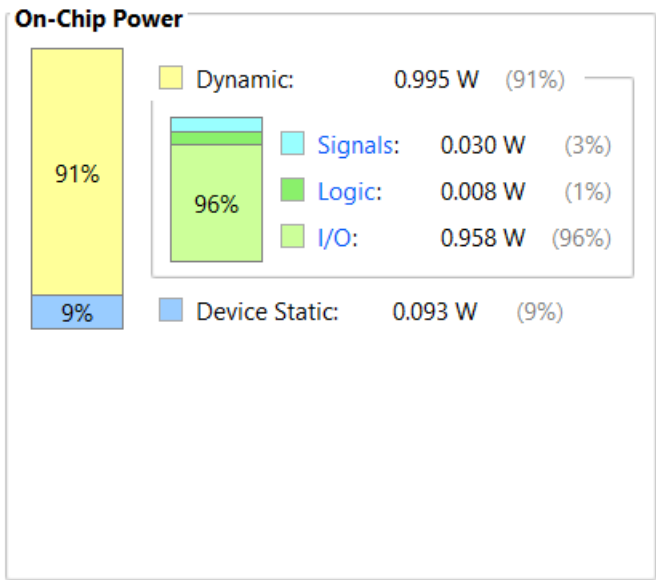[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



## Q12 parallel in parallel out register

Verilog code:-

```
module pipo_shift_register #(parameter N=4) (  
    input clk,  
    input reset,  
    input [N-1:0] parallel_in,  
    output [N-1:0] parallel_out  
);  
  
    reg [N-1:0] shift_register;  
  
    always @(posedge clk or posedge reset) begin  
        if (reset)  
            shift_register <= 0;  
        else  
            shift_register <= parallel_in;  
        end  
  
    assign parallel_out = shift_register;
```

```
endmodule
```

Test bench:-

```
module testbench_pipo;
```

```
    parameter N = 4;
```

```
    parameter CLK_PERIOD = 10; // Clock period in time units
```

```
    reg clk;
```

```
    reg reset;
```

```
    wire [N-1:0] parallel_in;
```

```
    wire [N-1:0] parallel_out;
```

```
    pipo_shift_register #(N) uut (
```

```
        .clk(clk),
```

```
        .reset(reset),
```

```
        .parallel_in(parallel_in),
```

```
        .parallel_out(parallel_out)
```

```
    );
```

```
    always begin
```

```
#CLK_PERIOD / 2 clk = ~clk;
end

initial begin
    $display("PIPO Shift Register Testbench");

    clk = 0;
    reset = 1;
    parallel_in = 4'b0000;
    #CLK_PERIOD reset = 0;


    parallel_in = 4'b1010;
    #CLK_PERIOD parallel_in = 4'b0101;

    reset = 1;
    #CLK_PERIOD reset = 0;
    $display("Parallel Out: %b", parallel_out);
```

```
$finish;  
end
```

```
endmodule
```

RTLsynthesis:-

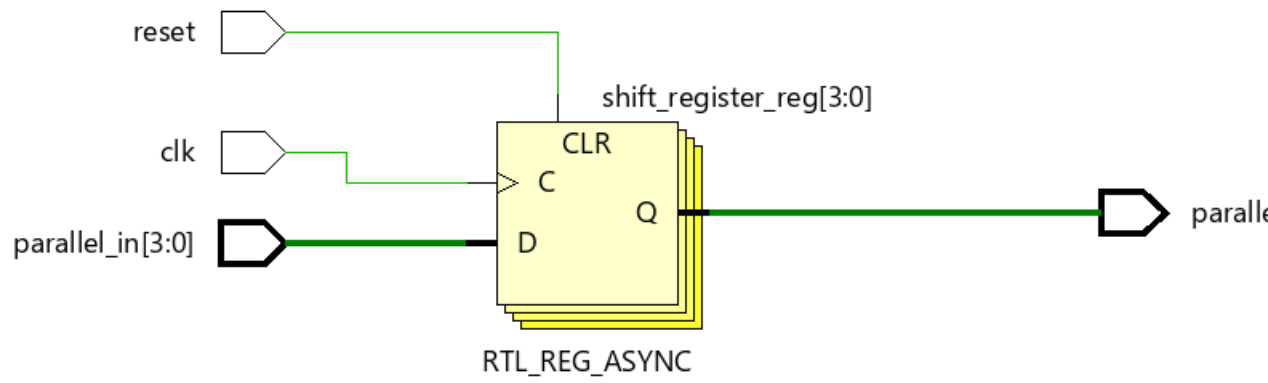

Synthesis report:-

## Start Writing Synthesis Report

### Report BlackBoxes:

BlackBox name	Instances

### Report Cell Usage:

Cell	Count
1	1
2	4
3	6
4	4

Finished Writing Synthesis Report : Time (s): cpu = 00:00:32 ; elapsed = 00:00:35 . Memory (MB):


## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>1.102 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>30.1°C</b>
Thermal Margin:	54.9°C (11.8 W)
Effective $\theta_{JA}$ :	4.6°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## Q13 parallel in serial out register

## Verilog code:-



```

module piso_shift_register #(parameter N=4) (
    input clk,
    input reset,
    input [N-1:0] parallel_in,
    output serial_out
);

    reg [N-1:0] shift_register;
    reg [N-1:0] temp;

    always @(posedge clk or posedge reset) begin
        if (reset)
            shift_register <= 0;
        else
            shift_register <= parallel_in;
    end

    always @(posedge clk or posedge reset) begin
        if (reset)
            temp <= 0;
        else
            temp <= {shift_register[N-2:0], temp[N-1]};
    end

```

end

assign serial\_out = temp[0];

endmodule

Test bench:-

module testbench\_piso;

parameter N = 4;

parameter CLK\_PERIOD = 10;

reg clk;

reg reset;

wire [N-1:0] parallel\_in;

wire serial\_out;

piso\_shift\_register #(N) uut (

.clk(clk),

```
.reset(reset),  
.parallel_in(parallel_in),  
.serial_out(serial_out)  
);
```

```
always begin  
    #CLK_PERIOD / 2 clk = ~clk;  
end
```

```
initial begin  
    $display("PISO Shift Register Testbench");
```

```
    clk = 0;  
    reset = 1;  
    parallel_in = 4'b0000;  
    #CLK_PERIOD reset = 0;
```

```
    parallel_in = 4'b1010;
```

```
#CLK_PERIOD parallel_in = 4'b0101;
```

```
reset = 1;
```

```
#CLK_PERIOD reset = 0;
```


```
$display("Serial Out: %b", serial_out);
```

```
$finish;
```

```
end
```

```
endmodule
```

RTLSynthesis:-

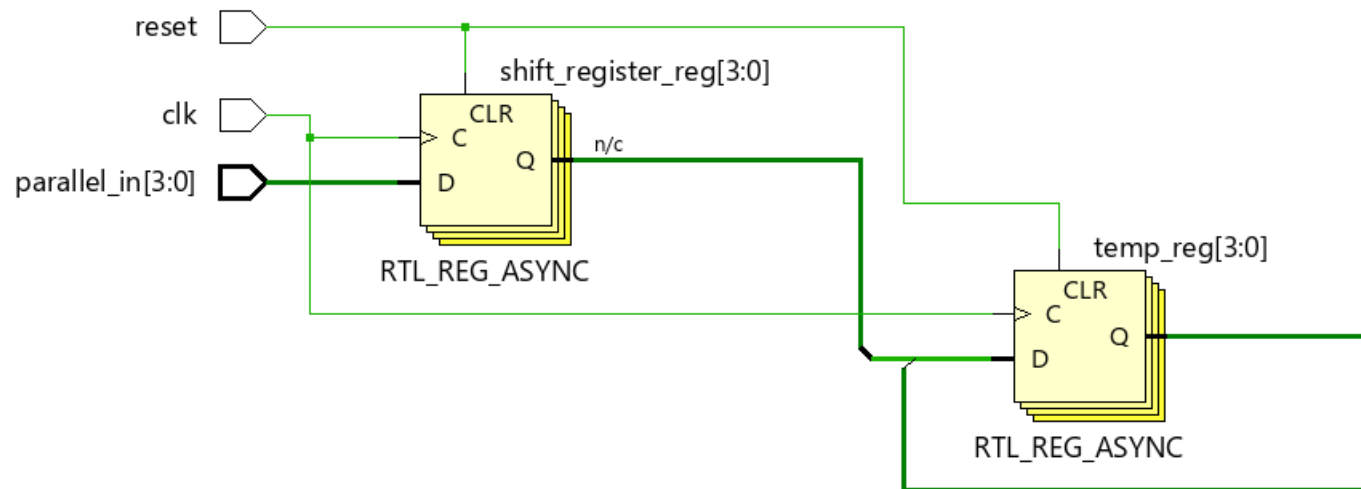

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+-----+
| BlackBox name | Instances |
+-----+-----+
+-----+-----+

```

Report Cell Usage:

```

+-----+-----+
| Cell | Count |
+-----+-----+
| 1 | BUFG | 1 |
| 2 | FDCE | 3 |
| 3 | IBUF | 3 |
| 4 | OBUF | 1 |
+-----+-----+


```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:21 ; elapsed = 00:00:24 . Memory (MB):
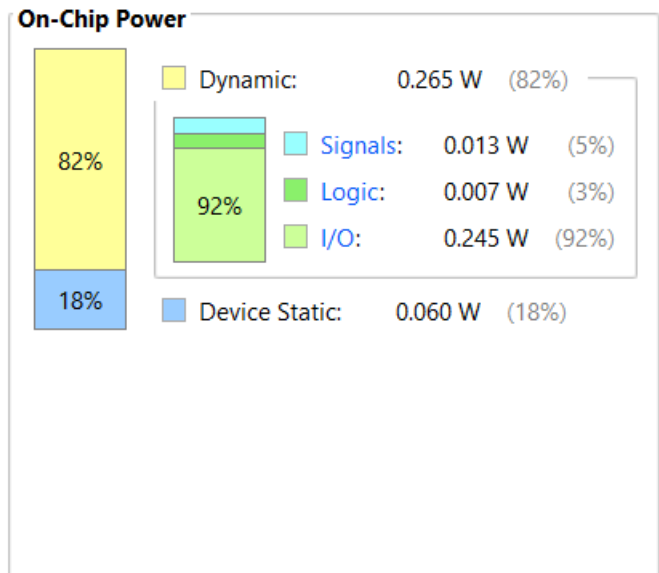
## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.325 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 26.7°C  
Thermal Margin: 73.3°C (13.9 W)  
Effective  $\theta_{JA}$ : 5.3°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



## Q14 Bidirectional Shift register:-

Verilog code:-

```
module bidirectional_shift_register #(parameter N=8) (  
    input clk,  
    input reset,  
    input shift_left,  
    input shift_right,  
    input [N-1:0] parallel_in,  
    output [N-1:0] parallel_out  
);
```

```

reg [N-1:0] shift_register;
reg [N-1:0] temp;

always @(posedge clk or posedge reset) begin
    if (reset)
        shift_register <= 0;
    else if (shift_left)
        shift_register <= {shift_register[N-2:0], 1'b0};
    else if (shift_right)
        shift_register <= {1'b0, shift_register[N-1:1]};
    else
        shift_register <= parallel_in;
end

assign parallel_out = shift_register;

endmodule

```

test bench:-

```

module testbench_bidirectional_shift_register;

```

```
parameter N = 8;
```

```
parameter CLK_PERIOD = 10;
```

```
reg clk;
```

```
reg reset;
```

```
reg shift_left;
```

```
reg shift_right;
```

```
wire [N-1:0] parallel_in;
```

```
wire [N-1:0] parallel_out;
```

```
bidirectional_shift_register #(N) uut (
```

```
    .clk(clk),
```

```
    .reset(reset),
```

```
    .shift_left(shift_left),
```

```
    .shift_right(shift_right),
```

```
    .parallel_in(parallel_in),
```

```
    .parallel_out(parallel_out)
```

```
);
```



```
always begin
```

```
    #CLK_PERIOD / 2 clk = ~clk;
```

```
end
```

```
initial begin
```

```
    $display("Bidirectional Shift Register Testbench");
```

```
    clk = 0;
```

```
    reset = 1;
```

```
    shift_left = 0;
```

```
    shift_right = 0;
```

```
    parallel_in = 8'b00000000;
```

```
    #CLK_PERIOD reset = 0;
```

```
    parallel_in = 8'b10101010;
```

```
    shift_left = 1;
```

```
    #CLK_PERIOD shift_left = 0;
```

```
shift_right = 1;
```

```
#CLK_PERIOD shift_right = 0;
```

```
shift_right = 1;
```

```
#CLK_PERIOD shift_right = 0;
```

```
parallel_in = 8'b11001100;
```

```
shift_left = 1;
```


```
#CLK_PERIOD shift_left = 0;
```

```
$display("Parallel Out: %b", parallel_out);
```

```
$finish;
```

```
end
```

RTLSynthesis :-

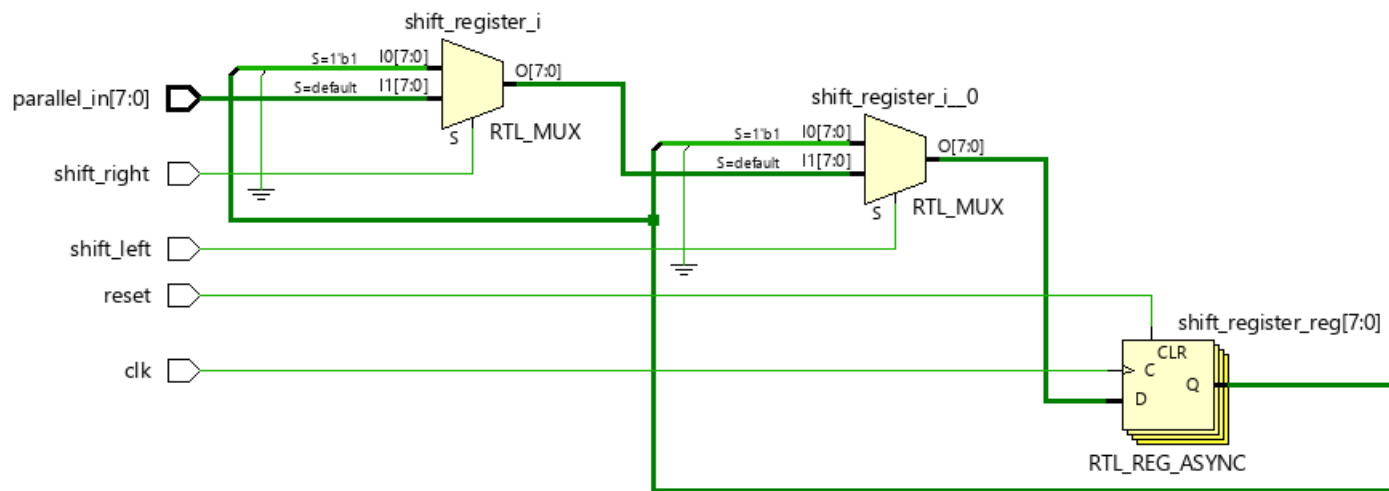

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

```

Report Cell Usage:

```

+-----+-----+
|      |Cell |Count |
+-----+-----+
| 1    |BUFG |    1|
| 2    |LUT4 |    2|
| 3    |LUT5 |    6|
| 4    |FDCE |    8|
| 5    |IBUF |   12|
| 6    |OBUF |    8|
+-----+-----+

```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:23 . Memory (MB):

## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** **4.127 W**  
**Design Power Budget:** **Not Specified**  
**Power Budget Margin:** **N/A**  
**Junction Temperature:** **46.7°C**  
Thermal Margin: 53.3°C (10.1 W)  
Effective  $\theta_{JA}$ : 5.3°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: **Low**  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## Q15 PRBS sequence generator

### Verilog code:-

```
module prbs_generator (  
    input clk,  
    input reset,  
    output reg [3:0] prbs_out  
);  
  
    reg [3:0] shift_register;
```

```
always @(posedge clk or posedge reset) begin
    if (reset)
        shift_register <= 4'b0001; // Initial seed value (non-zero)
    else
        shift_register <= {shift_register[2:0], shift_register[3] ^
shift_register[0]};
    end

    assign prbs_out = shift_register;

endmodule
```

Testbench:-

```
module testbench_prbs_generator;

    // Parameters
    parameter CLK_PERIOD = 10; // Clock period in time units

    // Signals
    reg clk;
```

```
reg reset;
wire [3:0] prbs_out;

// Instantiate the PRBS generator
prbs_generator uut (
    .clk(clk),
    .reset(reset),
    .prbs_out(prbs_out)
);

// Clock generation
always begin
    #CLK_PERIOD / 2 clk = ~clk;
end

// Testbench
initial begin
    $display("PRBS Generator Testbench");

    // Initialize
    clk = 0;
    reset = 1;
```

```
#CLK_PERIOD reset = 0;
```

```
// Generate and display PRBS sequence for 16 clock cycles
```

```
$display("PRBS Output:");
```

```
for (int i = 0; i < 16; i = i + 1) begin
```

```
    #CLK_PERIOD;
```

```
    $display("%b", prbs_out);
```


```
end
```

```
$finish;
```

```
end
```

```
endmodule
```

RTL synthesis:-

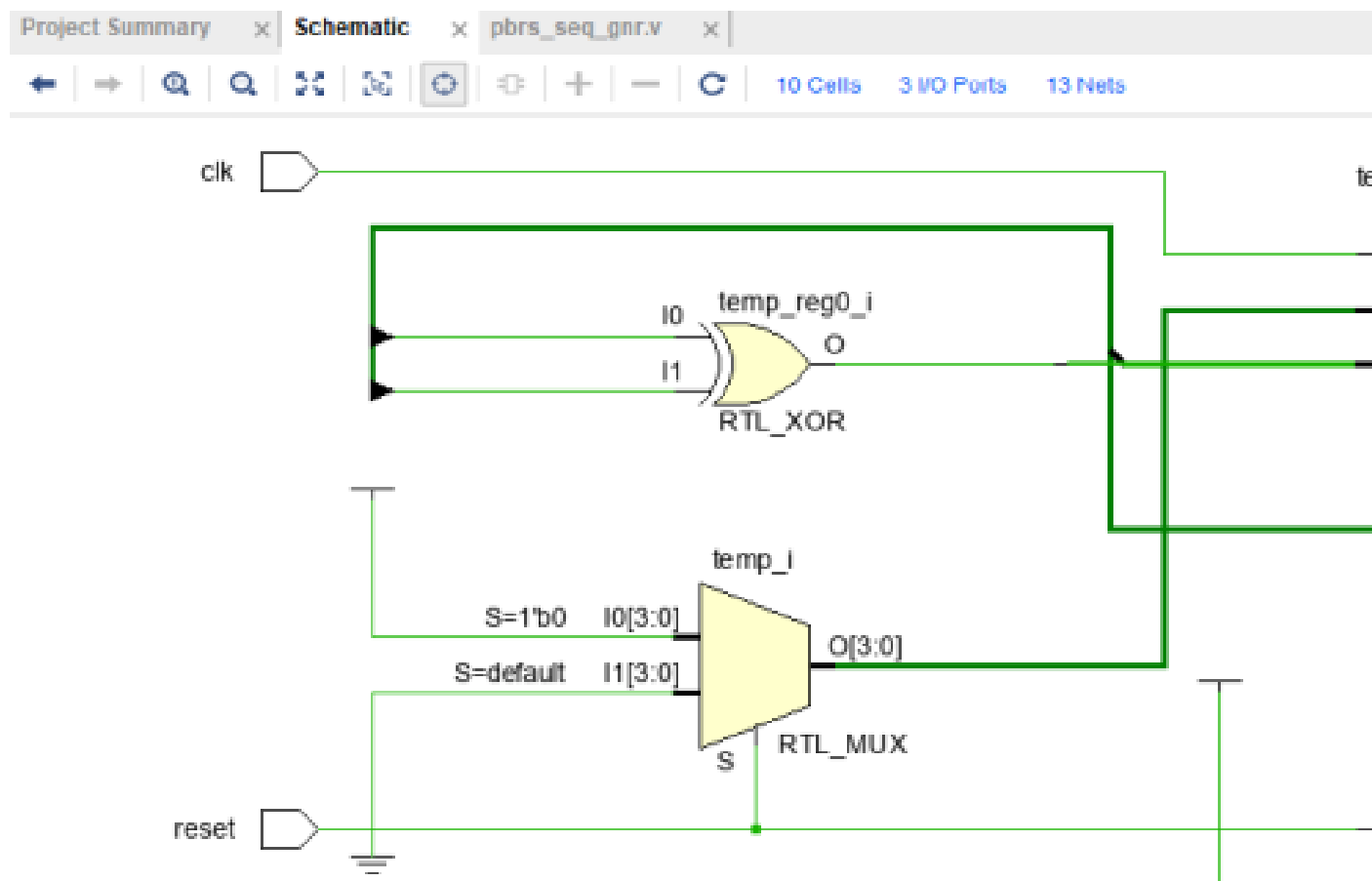

Synthesis report:-



-----  
Start Writing Synthesis Report  
-----

Report BlackBoxes:

```
+-----+-----+
| BlackBox name |Instances |
+-----+-----+
+-----+-----+
```

Report Cell Usage:

```
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |BUFG |    2|
|2      |LUT1 |    2|
|3      |LUT2 |    1|
|4      |FDRE |    8|
|5      |IBUF |    2|
|6      |OBUF |    1|
+-----+-----+
```

Report Instance Areas:

```
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |    16|
+-----+-----+-----+
```

-----  
Finished Writing Synthesis Report : Time (s): cpu = 00:00:09 ; elapsed = 00:00:16 . Memory (MB): peak = 1018.242 ; gain = 0.0  
-----


Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

<b>Total On-Chip Power:</b>	<b>0.1 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>25.2°C</b>
<b>Thermal Margin:</b>	<b>59.8°C (31.6 W)</b>
<b>Effective <math>\theta_{JA}</math>:</b>	<b>1.9°C/W</b>
<b>Power supplied to off-chip devices:</b>	<b>0 W</b>
<b>Confidence level:</b>	<b>Low</b>

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Q16 8-bit subtractor

Verilog code:-

```
module eight_bit_subtractor (  
    input [7:0] A,  
    input [7:0] B,  
    input borrow_in,  
    output [7:0] difference,  
    output borrow_out
```

);

wire [7:0] B\_complement;

assign B\_complement = (~B) + 1;

assign {borrow\_out, difference} = A + B\_complement +  
borrow\_in;

endmodule

Testbench:-

module testbench\_eight\_bit\_subtractor;

reg [7:0] A;

reg [7:0] B;

reg borrow\_in;

wire [7:0] difference;

wire borrow\_out;

```
eight_bit_subtractor uut (  
    .A(A),  
    .B(B),  
    .borrow_in(borrow_in),  
    .difference(difference),  
    .borrow_out(borrow_out)  
);
```

```
initial begin
```

```
    $display("8-Bit Subtractor Testbench");
```

```
    A = 8'b00001010;
```

```
    B = 8'b00000101;
```

```
    borrow_in = 1'b0;
```

```
    #10 $display("A = %b, B = %b, Borrow In = %b, Difference =  
%b, Borrow Out = %b", A, B, borrow_in, difference,  
borrow_out);
```

```
A = 8'b000000101;
B = 8'b00001010;
borrow_in = 1'b1;


#10 $display("A = %b, B = %b, Borrow In = %b, Difference =
%b, Borrow Out = %b", A, B, borrow_in, difference,
borrow_out);

$finish;

end

endmodule
```

RTL synthesis:-

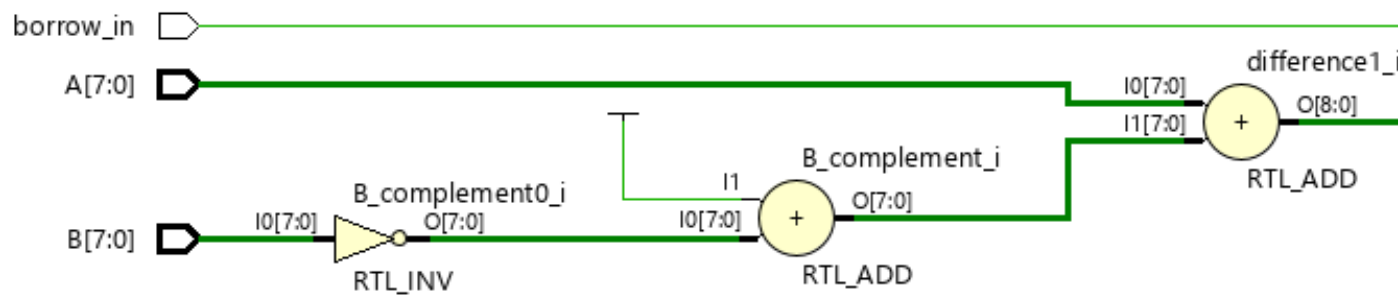

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+-----+
| |BlackBox name |Instances |
+-----+-----+
+-----+-----+
```

Report Cell Usage:

```
+-----+-----+
|      |Cell   |Count |
+-----+-----+
|1      |CARRY4  |    3 |
|2      |LUT2    |    1 |
|3      |LUT3    |    3 |
|4      |LUT4    |    2 |
|5      |LUT5    |    2 |
|6      |LUT6    |    2 |
|7      |IBUF    |   17 |
|8      |OBUF    |    9 |
+-----+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:23 . Memory (MB):

Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 6.518 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 65.3°C  
Thermal Margin: 34.7°C (5.6 W)  
Effective  $\theta_{JA}$ : 6.2°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low

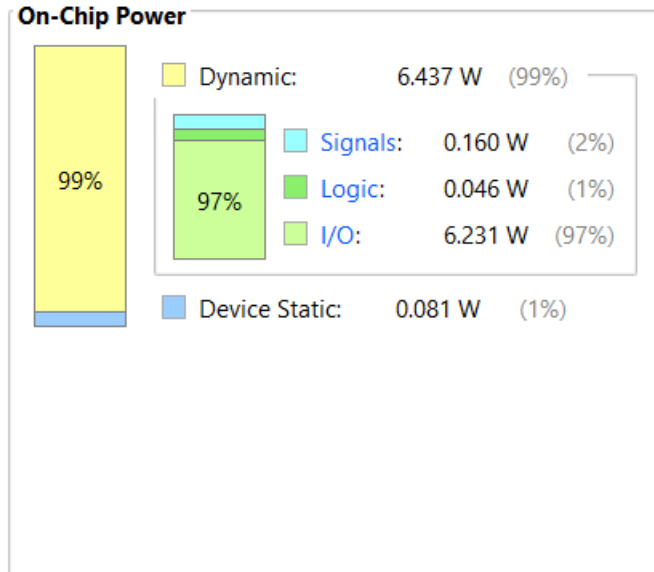[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q17 8-bit adder and subtractor

Verilog code:-

```
module addsub(A, B, OPER, RES);  
input OPER;  
input [7:0] A;  
input [7:0] B;  
output [7:0] RES;  
reg [7:0] RES;  
  
always @(A or B or OPER)  
begin
```



```
    if (OPER==1'b0) RES = A + B;
    else      RES = A - B;
end
endmodule
```

Testbench:-

```
module testbench_eight_bit_adder_subtractor;
```

```
// Signals
```

```
reg [7:0] A;
```

```
reg [7:0] B;
```

```
reg subtract;
```

```
wire [7:0] result;
```

```
wire overflow;
```

```
// Instantiate the adder/subtractor
```

```
eight_bit_adder_subtractor uut (
```

```
    .A(A),
```

```
    .B(B),
```

```
    .subtract(subtract),
```

```
.result(result),  
.overflow(overflow)  
);
```

```
// Testbench
```

```
initial begin
```

```
    $display("8-Bit Adder/Subtractor Testbench");
```

```
    // Test 1: A = 10, B = 5, subtract = 0
```

```
    A = 8'b00001010;
```

```
    B = 8'b00000101;
```

```
    subtract = 1'b0;
```

```
    #10 $display("A = %b, B = %b, Subtract = %b, Result = %b,  
Overflow = %b", A, B, subtract, result, overflow);
```

```
    // Test 2: A = 5, B = 10, subtract = 1
```

```
    A = 8'b00000101;
```

```
    B = 8'b00001010;
```


```
    subtract = 1'b1;
```

```
    #10 $display("A = %b, B = %b, Subtract = %b, Result = %b,  
Overflow = %b", A, B, subtract, result, overflow);
```

```
$finish;  
end
```

```
endmodule
```

RTL synthesis:-

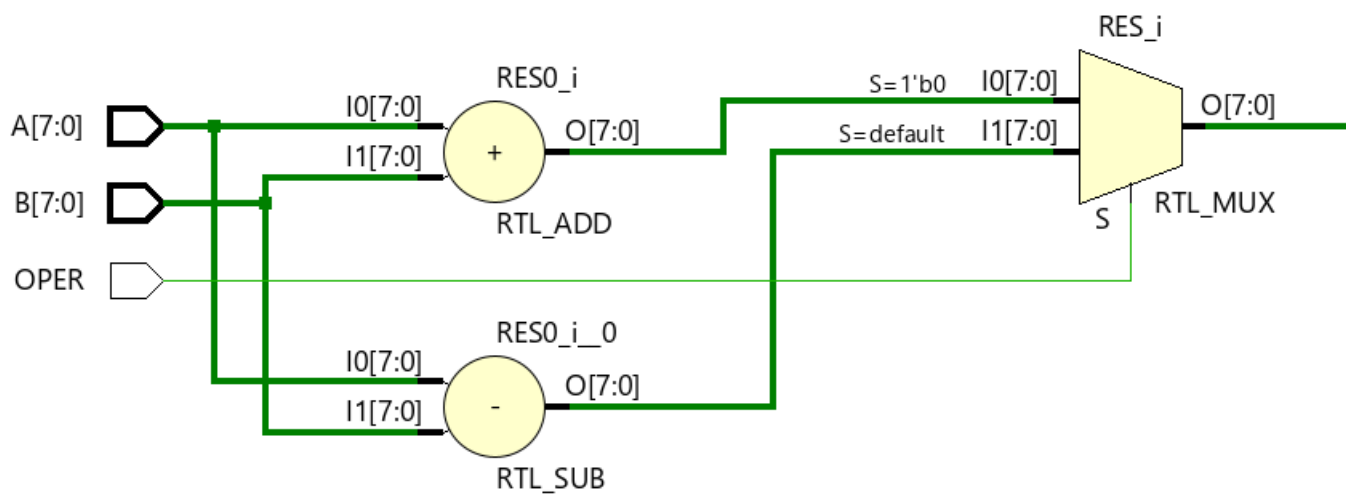

Synthesis report:-

-----  
Start Writing Synthesis Report  
-----

Report BlackBoxes:

```
+-----+
| |BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+-----+
|      |Cell      |Count |
+-----+-----+
|1      |CARRY4      |2      |
|2      |LUT1        |1      |
|3      |LUT3        |7      |
|4      |IBUF        |17     |
|5      |OBUF        |8      |
+-----+-----+
```


-----  
Finished Writing Synthesis Report : Time (s): cpu = 00:00:21 ; elapsed = 00:00:23 . Memory (MB):  
-----

## Power report:-

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** **6.099 W**  
**Design Power Budget:** **Not Specified**  
**Power Budget Margin:** **N/A**  
**Junction Temperature:** **55.5°C**  
Thermal Margin: 29.5°C (5.9 W)  
Effective  $\theta_{JA}$ : 5.0°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: **Low**

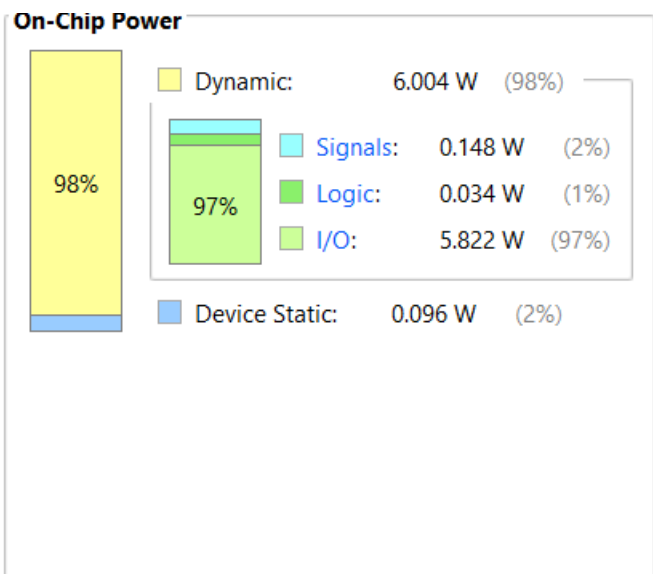[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



## Q18 4 bit multiplexer

Verilog code:-

```
module four_bit_multiplier (  
    input [3:0] A,  
    input [3:0] B,  
    output [7:0] product  
);  
  
    wire [7:0] temp_product;  
  
    assign temp_product = {4'b0, A} * {4'b0, B};  
    assign product = temp_product[7:0];  
  
endmodule
```

Testbench:-

```
module testbench_four_bit_multiplier;  
  
    reg [3:0] A;
```

```
reg [3:0] B;  
wire [7:0] product;
```

```
four_bit_multiplier uut (  
    .A(A),  
    .B(B),  
    .product(product)  
);
```

```
initial begin  
    $display("4-Bit Multiplier Testbench");
```

```
    A = 4'b0111;  
    B = 4'b0101;  
    #10 $display("A = %b, B = %b, Product = %b", A, B,  
product);
```

```
    A = 4'b0011;
```

```
B = 4'b1000;
```


```
#10 $display("A = %b, B = %b, Product = %b", A, B,  
product);
```

```
$finish;
```

```
end
```

```
endmodule
```

RTLsynthesis:-

 

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+-----+
|      |Cell  |Count |
+-----+-----+
|1      |CARRY4 |    2|
|2      |LUT2   |    3|
|3      |LUT3   |    1|
|4      |LUT4   |    4|
|5      |LUT5   |    1|
|6      |LUT6   |   10|
|7      |IBUF   |    8|
|8      |OBUF   |    8|
+-----+-----+
```


Finished Writing Synthesis Report : Time (s): cpu = 00:00:19 ; elapsed = 00:00:24 . Memory (MB):
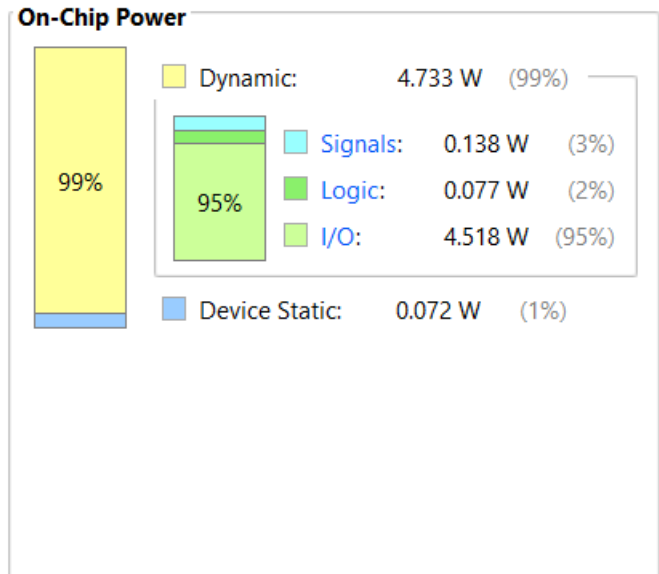
## Power report:-



Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 4.804 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 54.7°C  
Thermal Margin: 70.3°C (11.2 W)  
Effective  $\theta_{JA}$ : 6.2°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



## Q19 Fixed point division

Verilog code:-

```
module fixed_point_division (  
    input [15:0] dividend, // 16-bit input with 8 fractional bits  
    input [7:0] divisor, // 8-bit input with 8 fractional bits  
    output [15:0] quotient // 16-bit output with 8 fractional bits  
);
```

```
    reg [15:0] remainder;  
    reg [15:0] temp_quotient;  
    reg [7:0] count;
```

```
    always @(posedge clk or posedge reset) begin
```

```
if (reset) begin
    count <= 0;
    remainder <= 0;
    temp_quotient <= 0;
end
else begin
    if (remainder >= divisor) begin
        remainder <= remainder - divisor;
        temp_quotient <= temp_quotient + 1;
    end
    else begin
        remainder <= remainder;
        temp_quotient <= temp_quotient;
    end
end

count <= count + 1;
if (count == 7) begin
    quotient <= temp_quotient;
    count <= 0;
end
end
end
```

```
endmodule
```

```
test bench
```

```
module testbench_fixed_point_division;
```

```
    // Signals
```

```
    reg clk;
```

```
    reg reset;
```

```
    reg [15:0] dividend;
```

```
    reg [7:0] divisor;
```

```
    wire [15:0] quotient;
```

```
    // Instantiate the fixed-point division module
```

```
    fixed_point_division uut (
```

```
        .dividend(dividend),
```

```
        .divisor(divisor),
```

```
        .quotient(quotient)
```

```
    );
```

```
    // Clock generation
```

```
always begin
```

```
    #10 clk = ~clk;
```

```
end
```

```
// Testbench
```

```
initial begin
```

```
    $display("Fixed-Point Division Testbench");
```

```
// Initialize
```

```
clk = 0;
```

```
reset = 0;
```

```
dividend = 16'b0101100010000000; // Represents 13.25
```

```
divisor = 8'b00000100;           // Represents 0.25
```

```
// Apply reset
```

```
reset = 1;
```

```
#20 reset = 0;
```

```
// Provide inputs
```

```
dividend = 16'b0101100010000000; // Represents 13.25
```

```
divisor = 8'b00000100;           // Represents 0.25
```

```
#20;
```

```

// Display results
$display("Dividend: %d, Divisor: %d", dividend, divisor);

$display("Quotient: %d.%02d", quotient[15:8],
quotient[7:0]);


$finish;

end

endmodule

```

RTL symetic:-

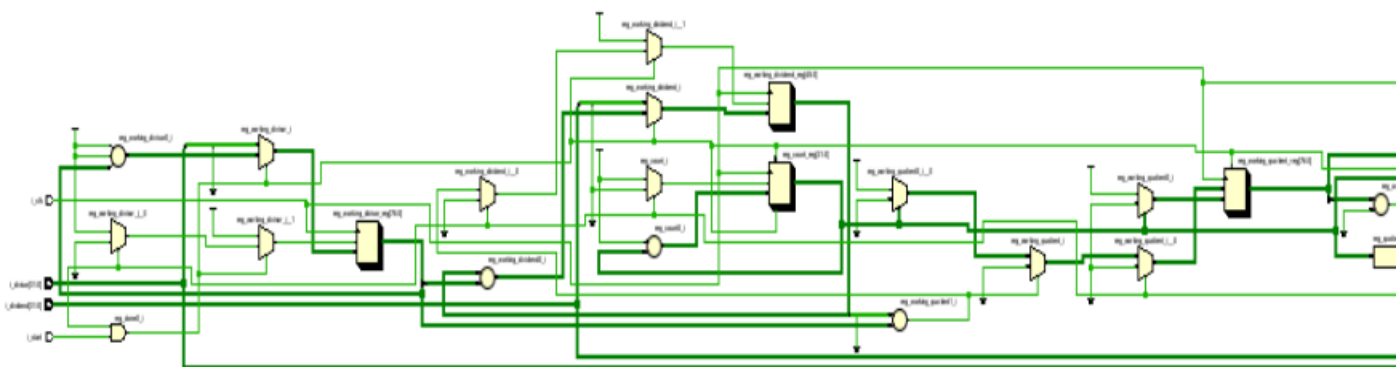

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+-----+-----+
|      |Cell  |Count |
+-----+-----+-----+
|1      |BUFG  |    1|
|2      |CARRY4|   30|
|3      |LUT1  |   34|
|4      |LUT2  |   20|
|5      |LUT3  |  121|
|6      |LUT4  |  102|
|7      |LUT5  |   39|
|8      |LUT6  |   27|
|9      |FDRE  |  261|
|10     |FDSE  |    4|
|11     |IBUF  |   66|
|12     |OBUF  |   34|
+-----+-----+-----+
```

Report Instance Areas:

```
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |  739|
+-----+-----+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:30 . Memory (MB): peak = 1019.531 ; gain = 0.  
/


Powerreport:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

<b>Total On-Chip Power:</b>	<b>2.475 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>29.7°C</b>
Thermal Margin:	55.3°C (29.2 W)
Effective $\theta_{JA}$ :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

#### On-Chip Power

 

Q20 Master slave jk flip flop

Verilogcode:-

```

module jk_flip_flop_master_slave(Q, Qn, C, J, K, RESETn);
    output Q;
    output Qn;
    input C;
    input J;
    input K;
    input RESETn;

    wire MQ;
    wire MQn;
    wire Cn;
    wire J1;
    wire K1;
    wire J2;
    wire K2;
    assign J2 = !RESETn ? 0 : J1;
    assign K2 = !RESETn ? 1 : K1;

    and(J1, J, Qn);
    and(K1, K, Q);
    not(Cn, C);
    sr_latch_gated master(MQ, MQn, C, J2, K2);
    sr_latch_gated slave(Q, Qn, Cn, MQ, MQn);
endmodule

module sr_latch_gated(Q, Qn, G, S, R);
    output Q;
    output Qn;
    input G;
    input S;
    input R;

    wire S1;
    wire R1;

    and(S1, G, S);
    and(R1, G, R);
    nor(Qn, S1, Q);
    nor(Q, R1, Qn);
endmodule

```

Test bench:-



```

module JK_ff_tb;

reg C, J, K, RESEIn;

wire Q;
wire Qn;

jk_flip_flop_master_slave jkflipflop( .C(C), .RESEIn(RESEIn), .J(J), .K(K), .Q(Q), .Qn(Qn) );

initial begin
    $dumpfile("dump.vcd"); $dumpvars;
    $monitor(C,J,K,Q,Qn,RESEIn);

    J = 1'b0;
    K = 1'b0;
    RESEIn = 1;
    C=1;

    #10
    RESEIn=0;
    J=1'b1;
    K=1'b0;

    #100
    RESEIn=0;
    J=1'b0;
    K=1'b1;

    #100
    RESEIn=0;
    J=1'b1;
    K=1'b1;

    #100
    RESEIn=0;

    #100
    RESEIn=0;
    J=1'b1;
    K=1'b1;

    #100
    RESEIn=0;
    J=1'b0;
    K=1'b0;


    #100
    RESEIn=1;
    J=1'b1;
    K=1'b0;

end
    always #25 C <= ~C;

endmodule

```

RTLsymetic:-

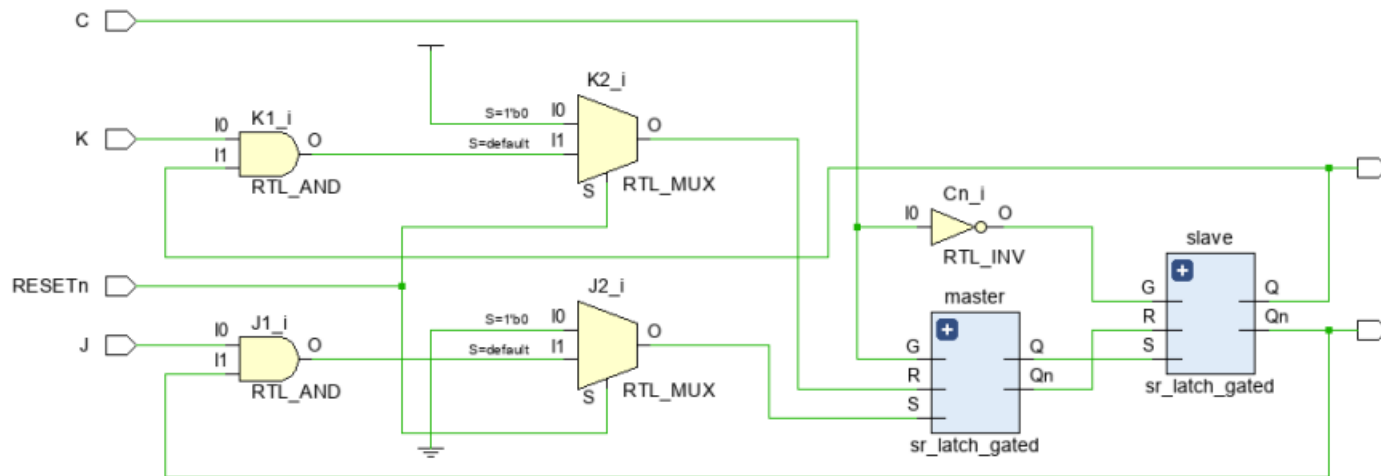

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

	Cell	Count
1	LUT3	2
2	LUT6	2
3	IBUF	4
4	OBUF	2

Report Instance Areas:


	Instance	Module	Cells
1	top		10

Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:28 . Memory (MB): peak = 1015.500 ; gain = 0.0
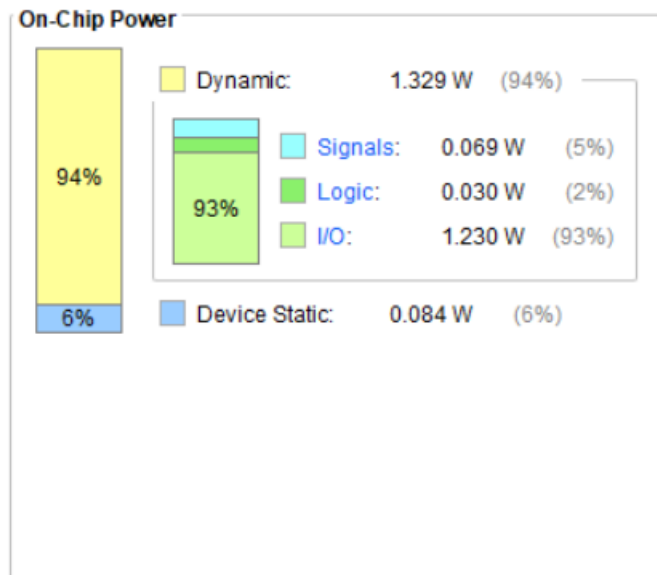
## Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** **1.413 W**  
**Design Power Budget:** **Not Specified**  
**Power Budget Margin:** **N/A**  
**Junction Temperature:** **27.7°C**  
Thermal Margin: 57.3°C (30.2 W)  
Effective  $\theta_{JA}$ : 1.9°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: **Low**  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q21 Positive edge trigger

Verilog code:-

```

module pos_edge_detect(clk,nrst,din,dout);
input clk;
input nrst;
input din;
output dout;
reg d_ff;

always @(posedge clk or negedge nrst)
begin
if(!nrst)
d_ff<=1'b0;
else
d_ff<=din;
end
assign dout=din&&(d_ff^din);
endmodule

module d_ff(D,C,a);
input D;
input C;
output a;
reg a;
always @(posedge C)
begin
a <= D;
end
endmodule

```

Testbench:-

```

module tb;
    reg nrst;
    reg clk;
    reg din;
    wire dout;

    pos_edge_det ped0 ( .nrst(nrst),
                        .clk(clk),
                        .din(din), .dout(dout));


    always #5 clk = ~clk;

    initial begin
        clk <= 0;
        nrst <= 0;
        #15 nrst<= 1;
        #20 nrst<= 0;
        #15 nrst<= 1;
        #10 nrst <= 0;
        #20 $finish;
    end

    initial begin
        $dumpvars;
        $dumpfile("dump.vcd");
    end
endmodule

```

RTLsymatic:-

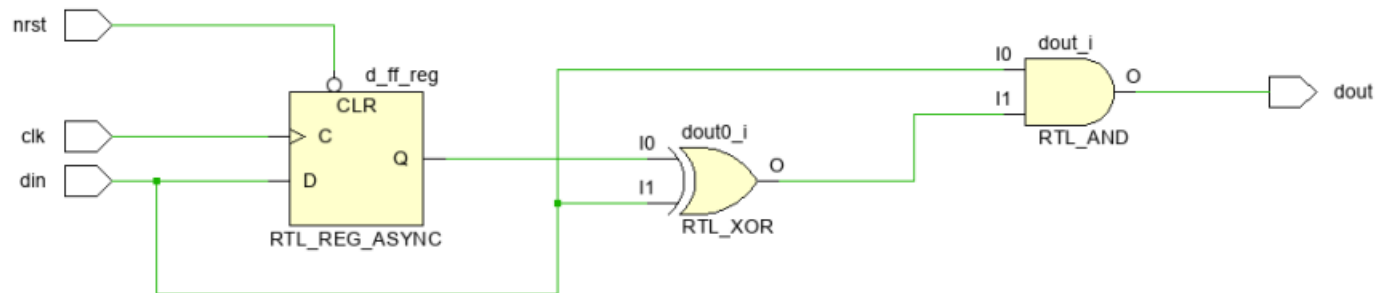

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
| BlackBox name | Instances |
+-----+

```

Report Cell Usage:

```

+-----+
| Cell | Count |
+-----+
| 1 | BUFG | 1 |
| 2 | LUT1 | 1 |
| 3 | LUT2 | 1 |
| 4 | FDCE | 1 |
| 5 | IBUF | 3 |
| 6 | OBUF | 1 |
+-----+

```

Report Instance Areas:

```

+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | 8 |
+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:41 . Memory (MB): peak = 1018.688 ; gain = 0.


## Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

<b>Total On-Chip Power:</b>	<b>0.339 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>25.6°C</b>
Thermal Margin:	59.4°C (31.3 W)
Effective $\theta_{JA}$ :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

#### On-Chip Power

 

Q22 Bcd adder

Verilog code:-

```

module bcd_adder(a,b,carry_in,sum,carry);

    input [3:0] a,b;
    input carry_in;
    output [3:0] sum;
    output carry;

    reg [4:0] sum_temp;
    reg [3:0] sum;
    reg carry;

    always @(a,b,carry_in)
    begin
        sum_temp = a+b+carry_in;
        if(sum_temp > 9)    begin
            sum_temp = sum_temp+6;
            carry = 1;
            sum = sum_temp[3:0];    end
        else    begin
            carry = 0;
            sum = sum_temp[3:0];
        end
    end

endmodule

```

Test bench:-



```

module tb_bcdadder;

    reg [3:0] a;
    reg [3:0] b;
    reg carry_in;

    wire [3:0] sum;
    wire carry;


    bcd_adder uut (
        .a(a),
        .b(b),
        .carry_in(carry_in),
        .sum(sum),
        .carry(carry)
    );

    initial begin

        a = 0;  b = 0;  carry_in = 0;  #100;
        a = 6;  b = 9;  carry_in = 0;  #100;
        a = 3;  b = 3;  carry_in = 1;  #100;
        a = 4;  b = 5;  carry_in = 0;  #100;
        a = 8;  b = 2;  carry_in = 0;  #100;
        a = 9;  b = 9;  carry_in = 1;  #100;
    end

```

RTLsymatic:-

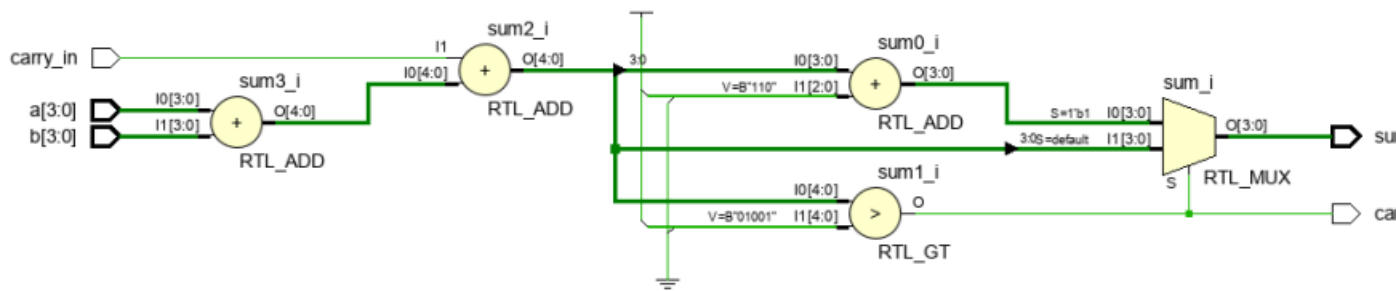

Symatic report:-

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
LUT3	1
LUT5	2
LUT6	4
IBUF	9
OBUF	5

Report Instance Areas:

Instance	Module	Cells
1	top	21


Finished Writing Synthesis Report : Time (s): cpu = 00:00:23 ; elapsed = 00:00:44 . Memory (MB): peak = 1016.285 ; gain = 0

Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

<b>Total On-Chip Power:</b>	<b>3.275 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>31.2°C</b>
<b>Thermal Margin:</b>	<b>53.8°C (28.4 W)</b>
<b>Effective <math>\theta_{JA}</math>:</b>	<b>1.9°C/W</b>
<b>Power supplied to off-chip devices:</b>	<b>0 W</b>
<b>Confidence level:</b>	<b>Low</b>

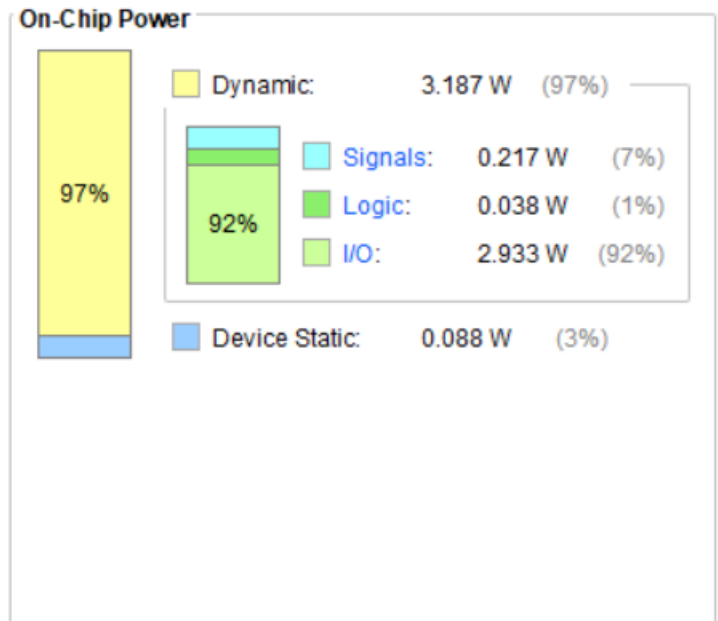[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q23 4 bit carry set

Verilog code:-

```

module carry_select_adder
    (   input [3:0] A,B,
        input cin,
        output [3:0] S,
        output cout
    );

    wire [3:0] temp0,temp1,carry0,carry1;

    fulladder fa00(A[0],B[0],1'b0,temp0[0],carry0[0]);
    fulladder fa01(A[1],B[1],carry0[0],temp0[1],carry0[1]);
    fulladder fa02(A[2],B[2],carry0[1],temp0[2],carry0[2]);
    fulladder fa03(A[3],B[3],carry0[2],temp0[3],carry0[3]);

    fulladder fa10(A[0],B[0],1'b1,temp1[0],carry1[0]);
    fulladder fa11(A[1],B[1],carry1[0],temp1[1],carry1[1]);
    fulladder fa12(A[2],B[2],carry1[1],temp1[2],carry1[2]);
    fulladder fa13(A[3],B[3],carry1[2],temp1[3],carry1[3]);

    multiplexer2 mux_carry(carry0[3],carry1[3],cin,cout);

    multiplexer2 mux_sum0(temp0[0],temp1[0],cin,S[0]);
    multiplexer2 mux_sum1(temp0[1],temp1[1],cin,S[1]);
    multiplexer2 mux_sum2(temp0[2],temp1[2],cin,S[2]);
    multiplexer2 mux_sum3(temp0[3],temp1[3],cin,S[3]);

endmodule

```

```

module fulladder
    (    input a,b,cin,
      output sum,carry
    );

    assign sum = a ^ b ^ cin;
    assign carry = (a & b) | (cin & b) | (a & cin);

endmodule

module multiplexer2
    (    input i0,i1,sel,
      output reg bitout
    );

    always@(i0,i1,sel)
    begin
        if(sel == 0)
            bitout = i0;
        else
            bitout = i1;
        end
    end

endmodule

```

TestBench:-

```

module tb_adder;

    reg [3:0] A;
    reg [3:0] B;
    reg cin;

    wire [3:0] S;
    wire cout;
    integer i,j,error;

    carry_select_adder uut (
        .A(A),
        .B(B),
        .cin(cin),
        .S(S),
        .cout(cout)
    );

    initial begin

        A = 0;
        B = 0;
        error = 0;

        cin = 0;
        for(i=0;i<16;i=i+1) begin
            for(j=0;j<16;j=j+1) begin
                A = i;
                B = j;
                #10;
                if((cout,S) != (i+j))


            end

            cin = 1;
            for(i=0;i<16;i=i+1) begin
                for(j=0;j<16;j=j+1) begin
                    A = i;
                    B = j;
                    #10;
                    if((cout,S) != (i+j+1))
                        error <= error + 1;
                end
            end
        end

    endmodule

```

RTLsymatic:-

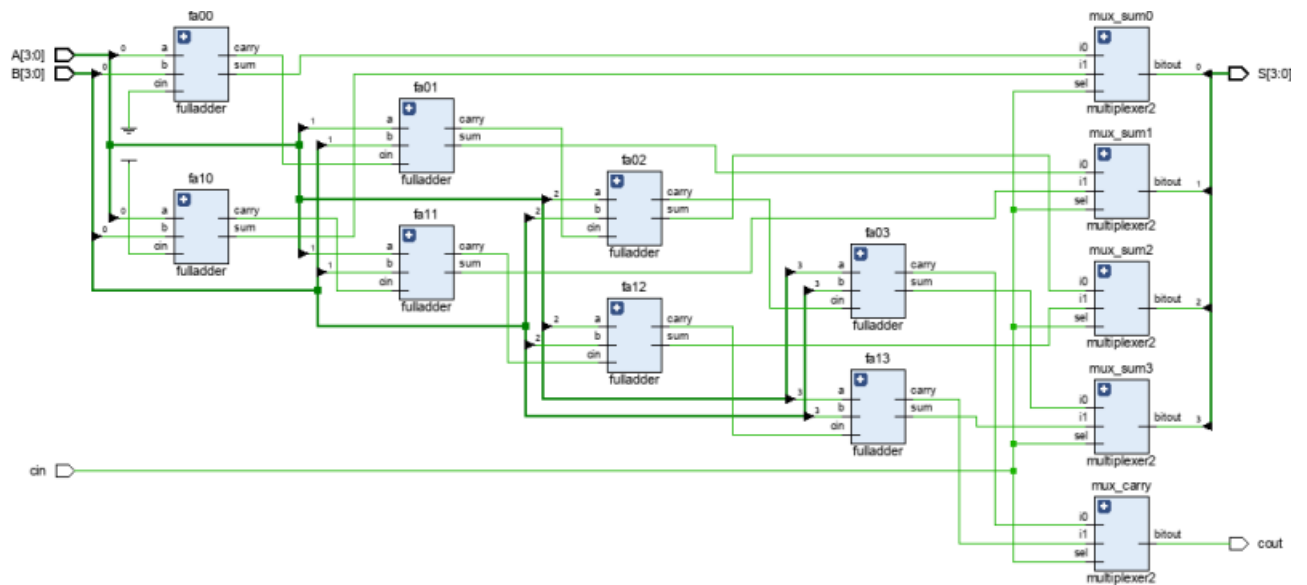

## Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```

+-----+
|BlackBox name|Instances|
+-----+

```

Report Cell Usage:

```

+-----+
|Cell|Count|
+-----+
|1|LUT3|2|
|2|LUT5|4|
|3|IBUF|9|
|4|OBUF|5|
+-----+

```

Report Instance Areas:

```

+-----+
|Instance|Module|Cells|
+-----+
|1|top|20|
+-----+


```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:22 ; elapsed = 00:00:43 . Memory (MB): peak = 1017.844 ; gain = 0.000
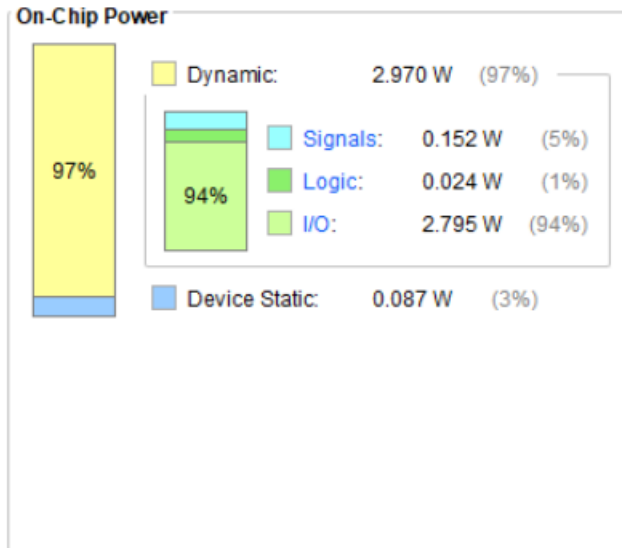
## Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** 3.058 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 30.8°C  
**Thermal Margin:** 54.2°C (28.6 W)  
**Effective  $\theta_{JA}$ :** 1.9°C/W  
**Power supplied to off-chip devices:** 0 W  
**Confidence level:** Low  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q24 More fsm 1010 sequence detector

Verilog code:-



```

module mor fsmolp(din, reset, clk, y);
input din;
input clk;
input reset;
output reg y;
reg [2:0] cst, nst;
parameter S0 = 3'b000,
           S1 = 3'b001,
           S2 = 3'b010,
           S3 = 3'b100,
           S4 = 3'b101;
always @(cst or din)
begin
case (cst)
S0: if (din == 1'b1)
begin
nst = S1;
y=1'b0;
end
else nst = cst;
S1: if (din == 1'b0)
begin
nst = S2;
y=1'b0;
end
else
begin
nst = cst;
y=1'b0;
end
S2: if (din == 1'b1)
begin
nst = S3;
y=1'b0;
end

```

---

```

S3: if (din == 1'b0)
    begin
        nst = S4;
        y=1'b0;
    end
    else
        begin
            nst = S1;
            y=1'b0;
        end
S4: if (din == 1'b0)
    begin
        nst = S1;
        y=1'b1;
    end
    else
        begin
            nst = S3;
            y=1'b1;
        end
    default: nst = S0;
endcase
end
always@(posedge clk)
begin
    if (reset)
        cst <= S0;
    else
        cst <= nst;
end
endmodule

```


Test bench:-

```

module morfsmolp_tb;
reg din,clk,reset;
wire y;
morfsmolp m1(din, reset, clk, y);
initial
begin
reset=0      ;clk=0;din=0;
$monitor($time, , , "c=%b",clk,, "y=%b",y,, "r=%b",reset,, "d=%b",din);
#10 din=1;
#10 din=0;
#10 din=1;
#10 din=0;
end
always
#5 clk=~clk;
initial
#100 $finish ;
endmodule

```

## RTLsymatic:-

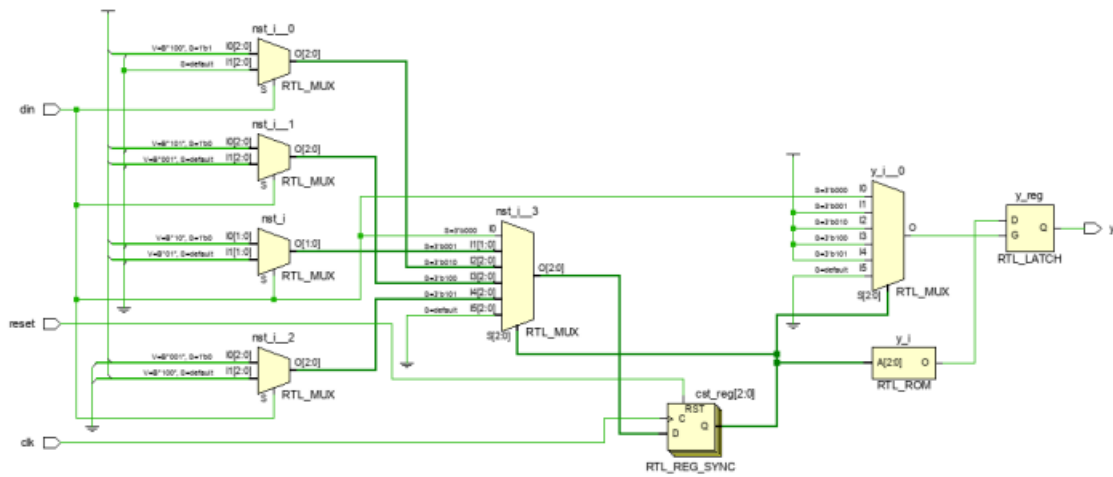

## Synthesis report:-

Start Writing Synthesis Report

---

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
```

Report Cell Usage:

```
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| LUT2 | 2|
|3| LUT3 | 2|
|4| LUT5 | 1|
|5| LUT6 | 1|
|6| FDRE | 4|
|7| FDSE | 1|
|8| LD | 1|
|9| IBUF | 3|
|10| OBUF | 1|
+-----+
```

Report Instance Areas:

```
+-----+
| Instance | Module | Cells |
+-----+
|1| top | | 17|
+-----+
```

---

Finished Writing Synthesis Report : Time (s): cpu = 00:00:10 ; elapsed = 00:00:17 . Memory (MB): peak = 1017.680 ; gain =


Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** 0.172 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.3°C  
 Thermal Margin: 59.7°C (31.5 W)  
 Effective  $\theta_{JA}$ : 1.9°C/W  
 Power supplied to off-chip devices: 0 W  
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

#### On-Chip Power

 

Q25 N X 1 mux

Verilog code:-

```
module mux_4_1(
    input [1:0] sel,
    input i0,i1,i2,i3,
    output reg y);

    always @(*) begin
        case(sel)
            2'h0: y = i0;
            2'h1: y = i1;
            2'h2: y = i2;
            2'h3: y = i3;
            default: $display("Invalid sel input");
        endcase
    end
endmodule
```

Test bench:-

```


module tb;
  reg [1:0] sel;
  reg i0,i1,i2,i3;
  wire y;

  mux_example mux(sel, i0, i1, i2, i3, y);

  initial begin
    $monitor("sel = %b -> i3 = %0b, i2 = %0b ,i1 = %0b, i0 = %0b -> y = %0b", sel,i3,i2,i1,i0,
    {i3,i2,i1,i0} = 4'h5;
    repeat(6) begin
      sel = $random;
      #5;
    end
  end
endmodule

```

RTL symatic:-

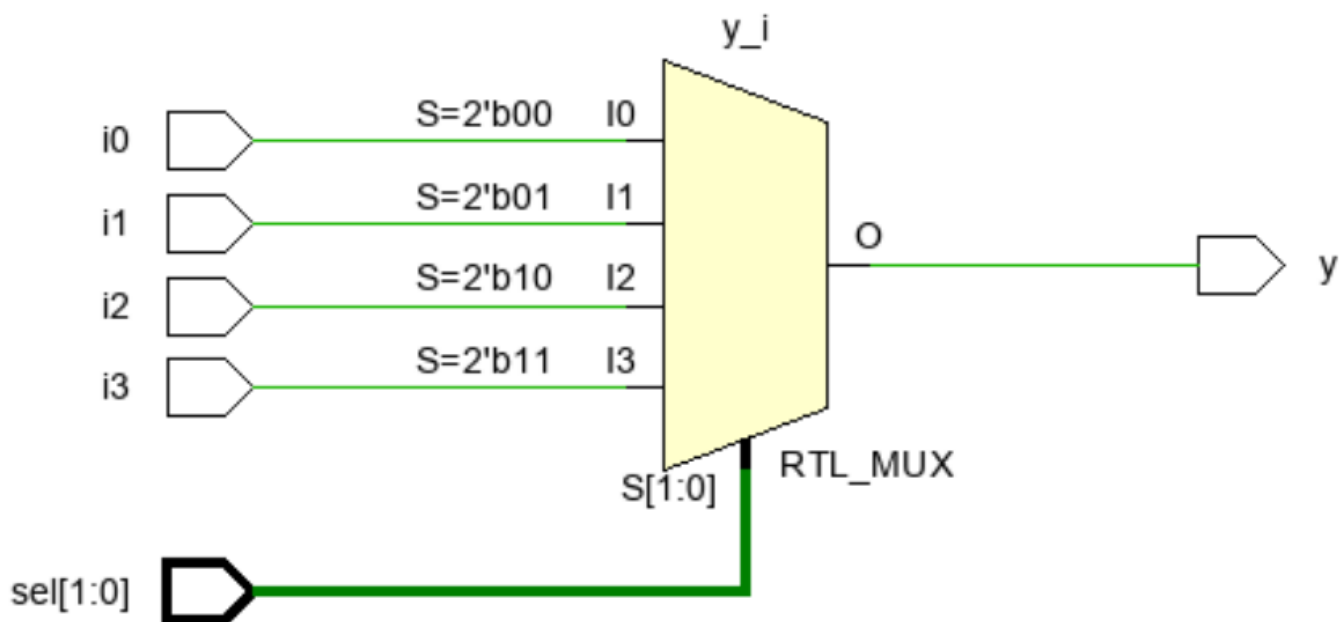

Synthesis report:-

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
```

Report Cell Usage:

```
+-----+
| Cell | Count |
+-----+
| 1 | LUT6 | 1 |
| 2 | IBUF | 6 |
| 3 | OBUF | 1 |
+-----+
```

Report Instance Areas:

```
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | 8 |
+-----+
```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:11 ; elapsed = 00:00:20 . Memory (MB): peak = 1020.262 ; gain

## Power report:-

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

**Total On-Chip Power:** 0.544 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 26.0°C  
Thermal Margin: 59.0°C (31.1 W)  
Effective  $\theta_{JA}$ : 1.9°C/W  
Power supplied to off-chip devices: 0 W  
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

